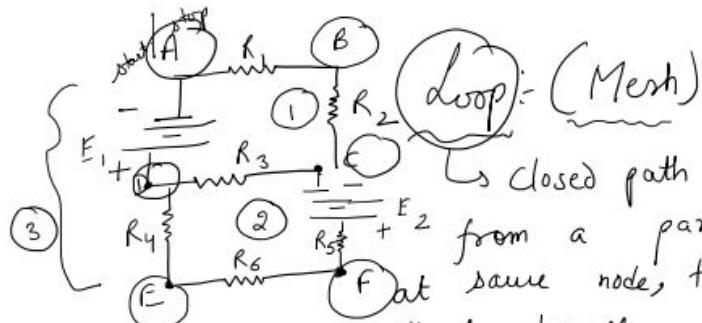


Network Analysis & Synthesis


Any arrangement of various electrical energy source along with different circuit elements is called an Electrical n/w



closed path which originates from a particular node, terminates at same node, travelling along various other nodes, without travelling through any node twice.

OR



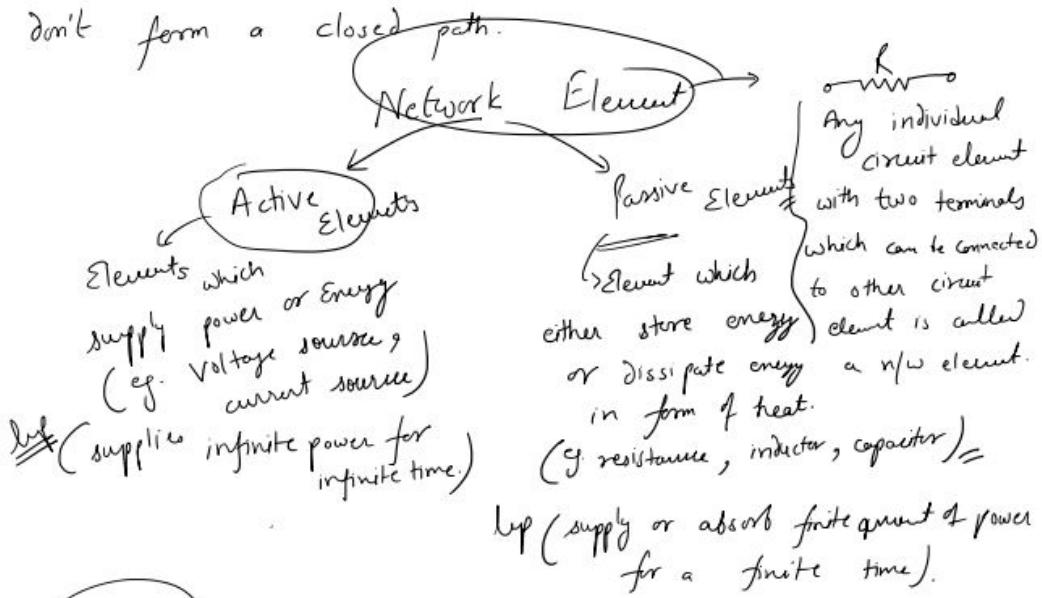
set of branches forming a closed path in a n/w in such a way that if one branch is removed then remaining branches don't form a closed path.




Branch:




Branch: AB ED

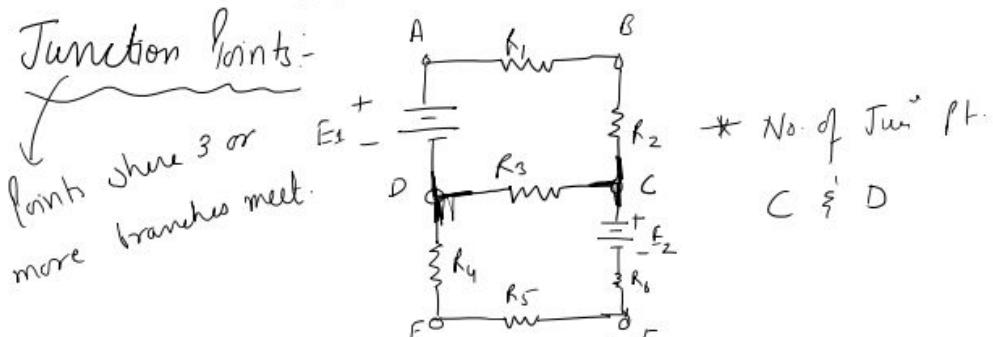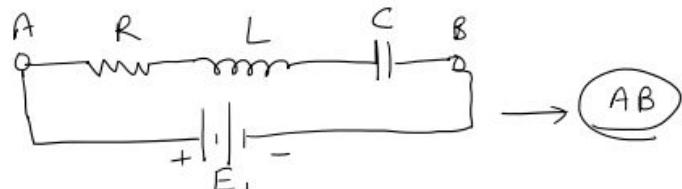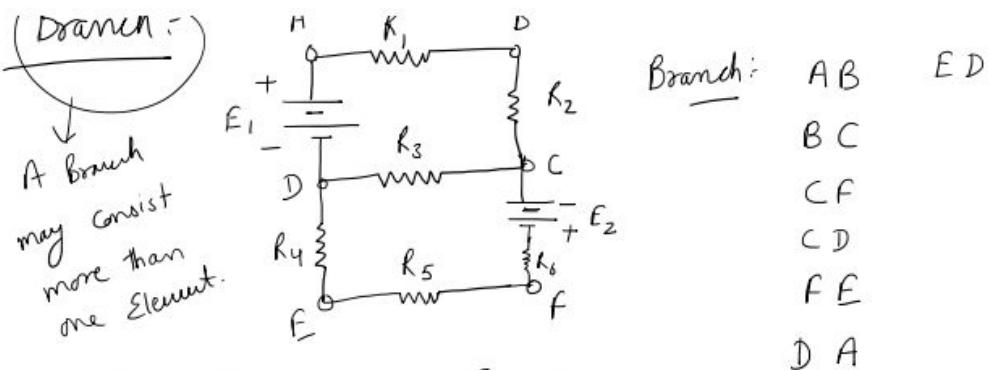

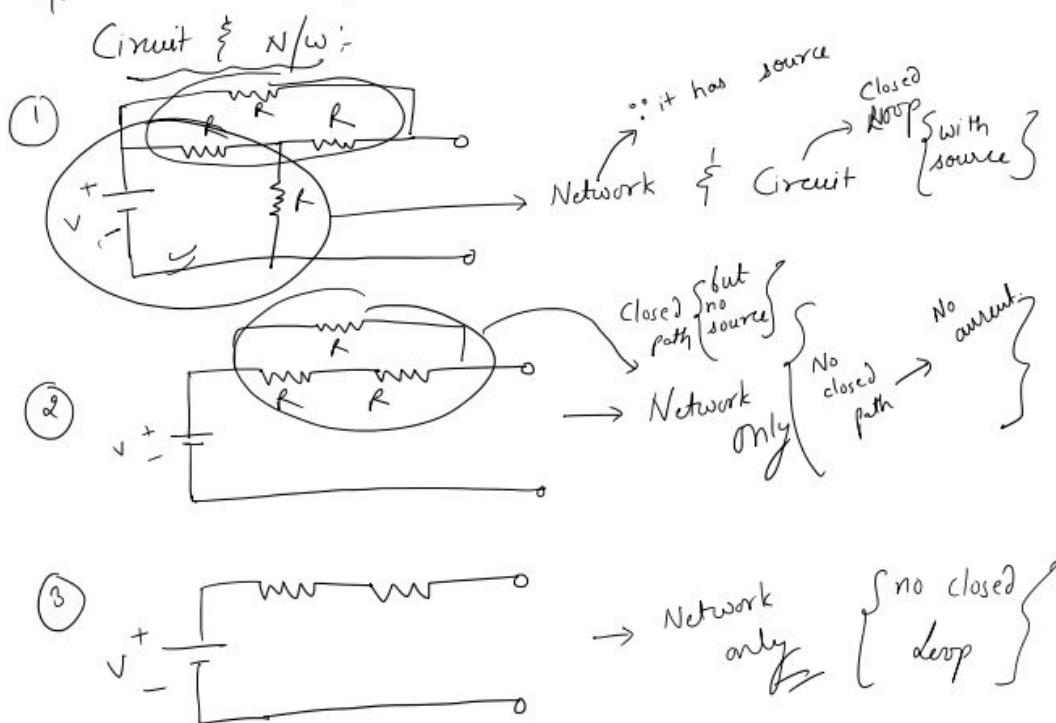
Node:- where 2 or more branches are joined together.
Points A, B, C, D, E, F \Rightarrow Nodes



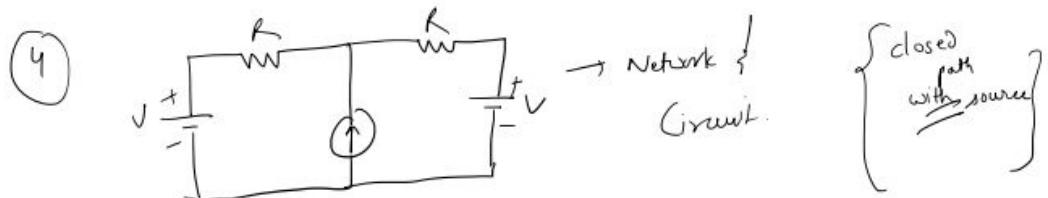

~~Def~~ Every circuit is a network but all n/w may not be circuit. → True.


* Degree of node:-

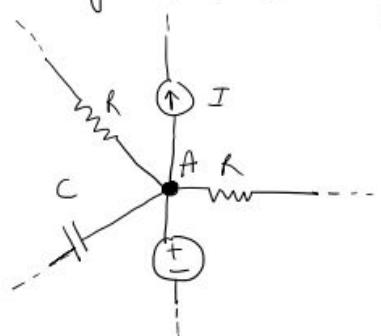

Number of branches connected to a node is called degree of node.

$$\text{Degree} = 5$$

Degree of Node = Branch Connected

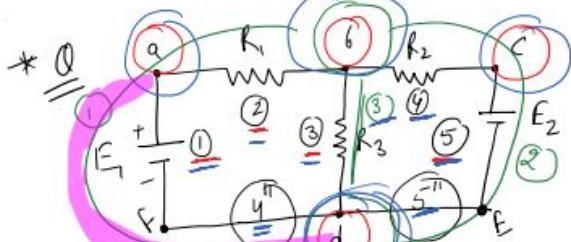

find no. of nodes & no. of branches?

$$(A) \quad n=4, b=5 \quad \{a, b, c, d\}$$


$$(B) \quad n=3, b=4 \quad \{a, b, d\} \quad \{c, f\}$$



$$(C) \quad n=2, b=3 \quad \{b, d\} \quad \{c, f\}$$

All of Above

~~Def~~ $\{b=n+1\} \rightarrow \{\text{branch} = \text{node} + 1\}$ → Not necessarily


* Q

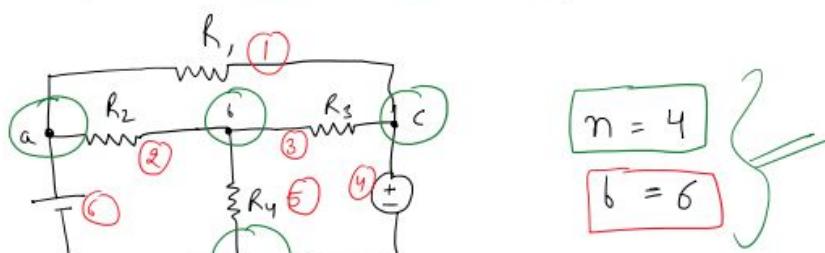

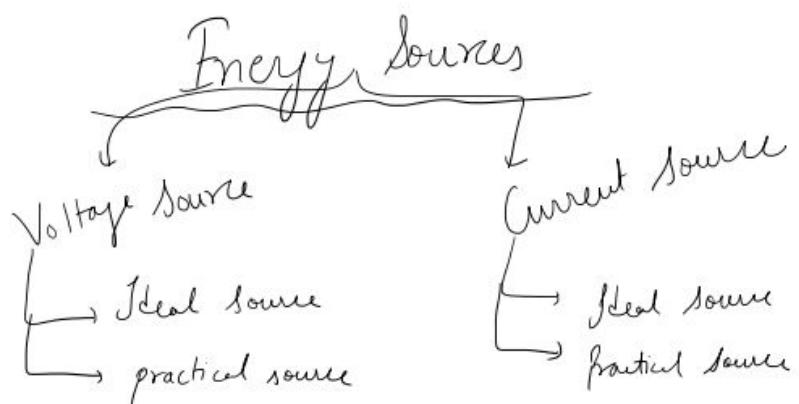
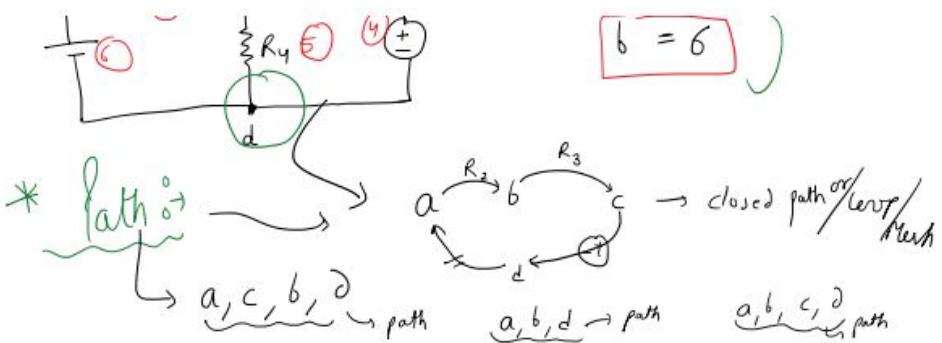


① Voltage source:-

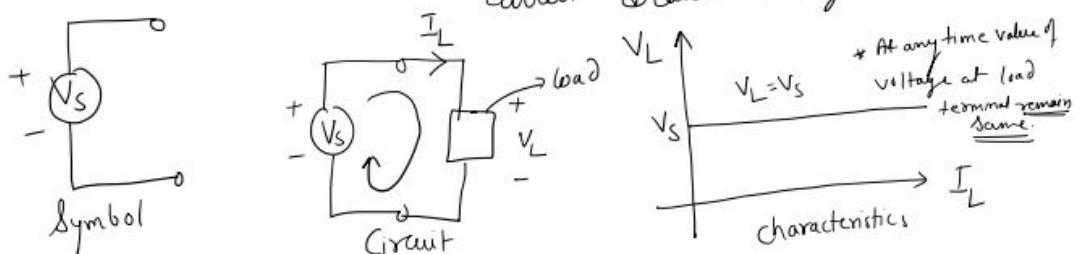ideal energy source which gives constant voltage across its terminals irrespective of current drawn through its terminal.




Practical Voltage source:-

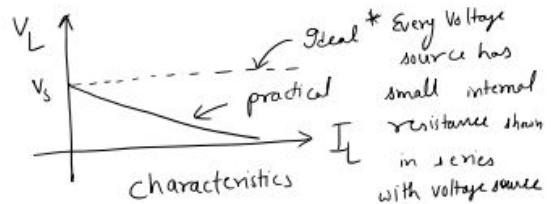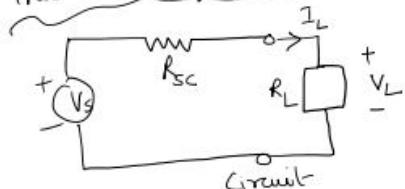

* If there is no load





$$I_L = 0, V = V_s$$
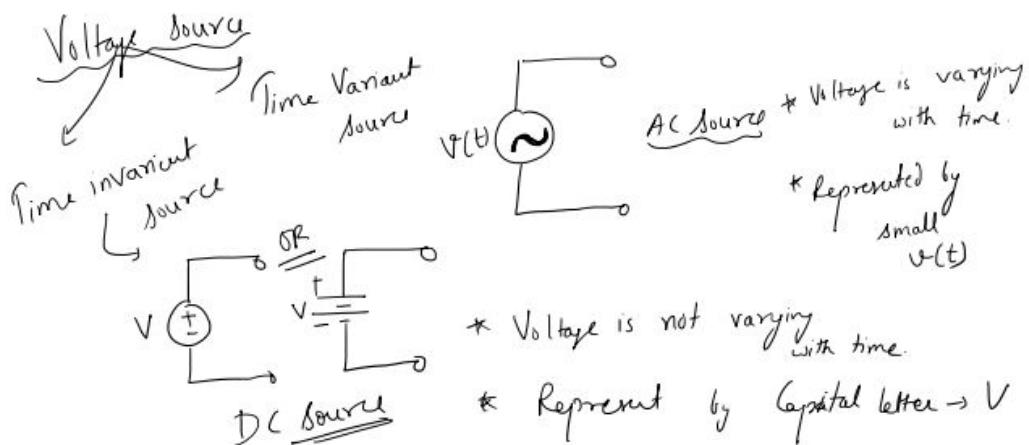
$$V_L = -R_{sc} I_L + V_s \quad \text{or} \quad V_L = V_s - I_L R_{sc} = \begin{cases} V = IR \\ V_{Rsc} = I_L R_{sc} \end{cases}$$



② Current Source: Ideal:

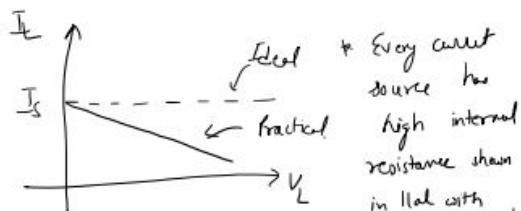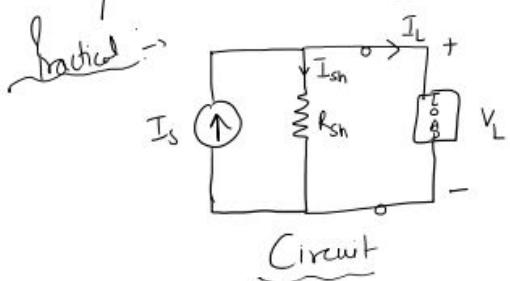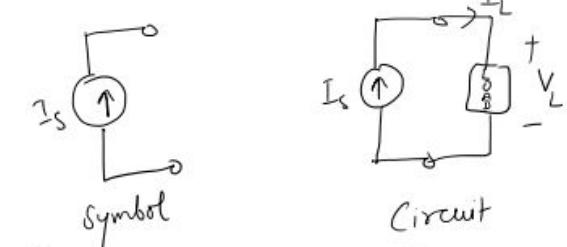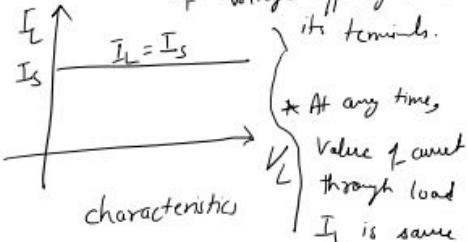* source which gives constant current at its terminal irrespective of voltage applied across its terminals.




$$\text{by } I_L + I_{sh} = I_S$$

$$\text{As } I_{sh} \uparrow \quad I_L \downarrow$$

$$I_L < I_S$$


$$R_{sh} = \infty$$

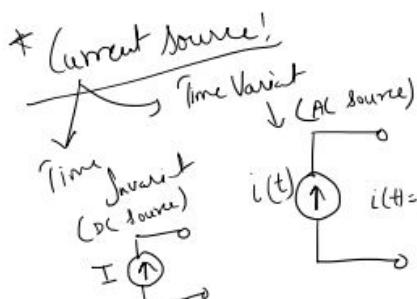


* for ideal current source $i(t) = A \sin \omega t$

Electrical Circuit Networks

(A) (B) (C) ... (D)

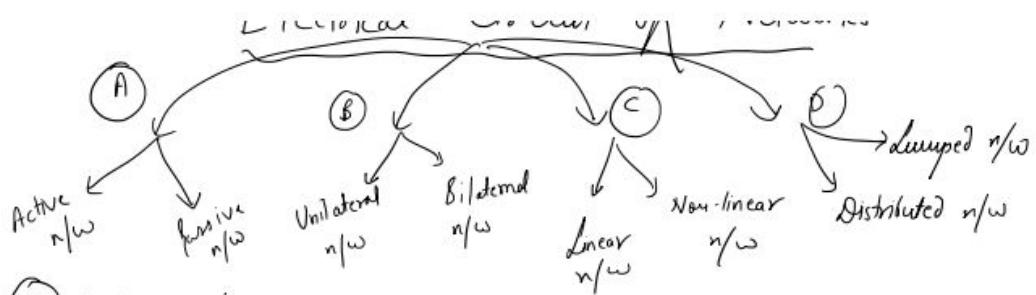


(1) Active N/W:-

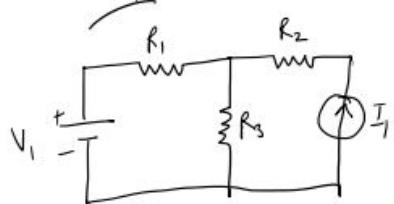

* A circuit having one source of energy
Voltage source Current source

Passive N/W :-

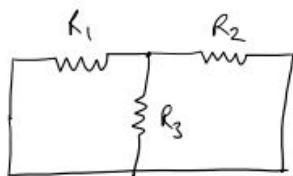

A circuit with no energy source (passive n/w or passive circuit)

(B) Unilateral N/W:- A circuit whose characteristics/behaviour is dependent on direction of current through various element. e.g. Diode

allow flow of current only in one direction
Unilateral Element or transistor

Bilateral N/W:-

e.g. Resistor

A circuit whose characteristics behaviour is same irrespective of direction of current through various elements (e.g. R, L, C) -

(C) Non-linear n/w:-


(C) Linear \nmid Non-linear n/w:-

A circuit/n/w whose parameter like, resistance, inductance, capacitance are always constant (irrespective of change in time, temp., voltage etc.)

* Ohm's Law $\xrightarrow{\text{can be applied}}$ to such n/w.


* Using law of superposition, mathematical eq^r of such n/w can be obtained.

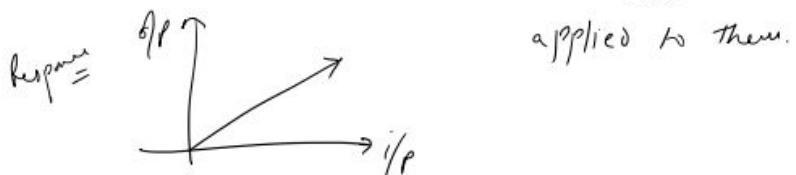* Response of various n/w element $\xrightarrow{\text{is linear wrt to excitation}}$



Non-linear n/w \rightarrow A circuit whose parameter changes with change in time, temp., voltage etc.

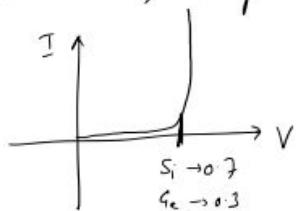Ckt having
diode
Current doesn't vary linearly with voltage applied to it.



* Ohm's Law $\xrightarrow{\text{may/not be}}$ applied to such n/w.

(4) Dumped Distributed n/w:-

A n/w in which all the n/w elements are physically separable. e.g. Most of electric n/w

↳ Dumped
having element R, L, C etc.

N/w in which ckt element (C, L, C) etc can't be physically separable.

e.g. Transmission lines Ω_1, r, n etc. Ω_2, L, C

L, C, R Transmission lines --- " physical separate".
R, L, C of T-line are distributed over complete length & can't be separate element.

- * Which is an ideal source?
- a) Resistor
 - b) Capacitor
 - c) Voltage source ✓
 - d) Op-amp. (operational amplifier) ✓

Q Which is non-linear element?

- a) Fuse
- b) Transistor
- c) Thermistor
- d) All of above ✓

Q Transistor/op-amp $\xrightarrow[\text{special case}]{\text{are}}$ of active element.

- * Linear Element \rightarrow which obey ohm's law. (R, L, C)
- * Non-linear Element \rightarrow which doesn't obey ohm's law (Diode)

* key points: It should not be considered that non-linear devices are undesirable elements.


Q ① Zener Diode: \rightarrow Nonlinear element \rightarrow Used in voltage regulation.

② Fuse: \rightarrow Non-linear element \rightarrow used for protecting from over current.

③ Thermistor: \rightarrow non-linear element \rightarrow used for all thermostat application.

Unilateral Element:

- ↳ Diode
- ↳ Transistor

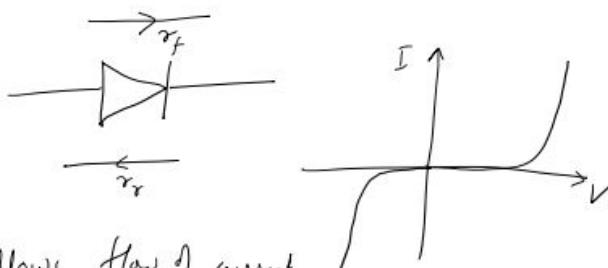


Element allows flow of current in one direction.


* Element whose parametric value is not constant with reversal of current.

Bilateral Element: \rightarrow Element allow flow of current in both directions

- ↳ e.g. R, L, C

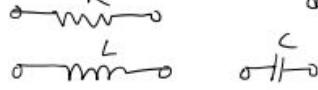


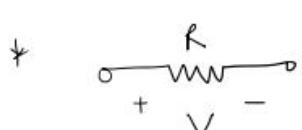* Elements whose parametric value doesn't change (constant) with reversal of current.



$$i = \frac{V}{R}$$

$i \propto V$

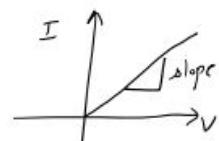

$$i = G_1 \cdot V$$

$$\text{or } G_1 = \frac{1}{R}$$


conductance.

$R \rightarrow \text{ohm}(\Omega)$

$G_1 \rightarrow \text{mho}(S)$

$$\text{slope} = \frac{dI}{dV} = \frac{1}{R}$$

$$\text{slope} = G_1$$

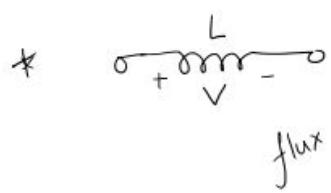



$$\oint \Phi \propto i$$

$$\Phi = L i$$

L Inductance (Henry (H))

$$V = L \frac{di}{dt}$$


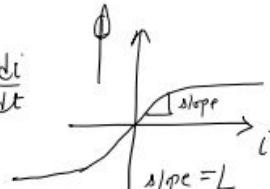


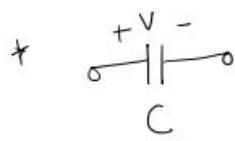

$$q \propto V$$

$$q = CV$$

$$i = \frac{dq}{dt} = C \frac{dV}{dt}$$

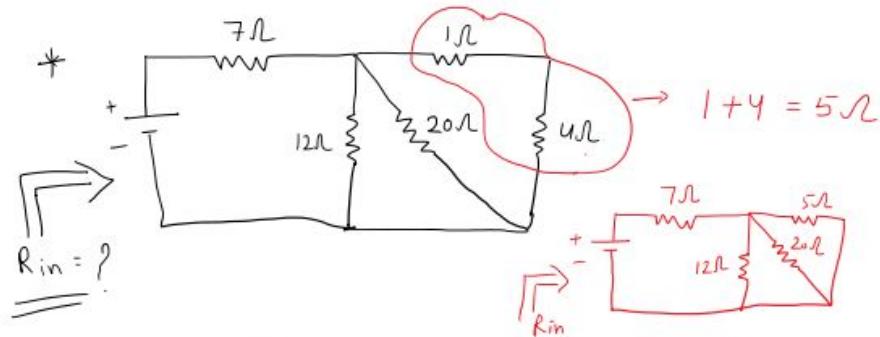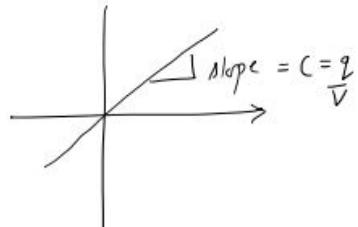


$$\begin{aligned} R_{in} &= \frac{7 \parallel 3}{R_1 R_2 / (R_1 + R_2)} \\ &= \frac{20 \times 5}{20 + 5} = \frac{100}{25} = 4 \quad (\text{Series}) \\ &\quad * \quad * \quad * \\ &= \frac{5 \times 20 \times 12}{5 + 20 + 12} = \frac{120}{37} = 3.243 \quad (\text{Parallel}) \\ &\quad * \quad * \quad * \\ &= \frac{12 \times 4}{12 + 4} = \frac{48}{16} = 3 \quad (\text{Parallel}) \end{aligned}$$

$$\begin{aligned} R_{in} &= \frac{3 \parallel 2}{R_1 R_2 / (R_1 + R_2)} \\ &= \frac{6 \parallel 4}{6 + 4} = 1 \quad (\text{Series}) \\ &\quad * \quad * \quad * \\ &= \frac{5 \parallel 10}{5 + 10} = \frac{5 \times 10}{15} = \frac{50}{15} = 3.33 \quad (\text{Parallel}) \end{aligned}$$

Analysis of Series Circuit:

Analysis of Series Circuit:

① Resistors in Series:

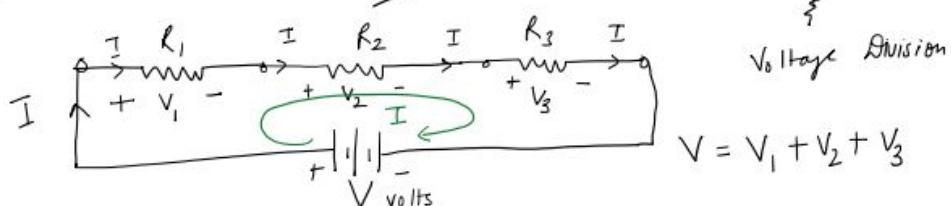

$$V_1 = IR_1, \quad V_2 = IR_2, \quad V_3 = IR_3$$

$$V = V_1 + V_2 + V_3 = IR_1 + IR_2 + IR_3$$



$$= I(R_1 + R_2 + R_3)$$

or

$$V = I R_{eq} \quad \text{where } R_{eq} = R_1 + R_2 + R_3$$

Total E_q resistance for n resistance in series of series circuit is $R_{eq} = R_1 + R_2 + R_3 + \dots + R_n = \sum_{i=1}^n R_i$

② Inductors in Series:

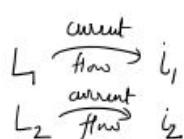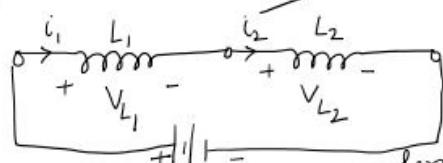

$$V_{L1} = L_1 \frac{di}{dt}$$

$$V_{L2} = L_2 \frac{di}{dt}$$

$$V_L = V_{L1} + V_{L2}$$

$$L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

$$\left. \begin{array}{l} + V_L - \\ + V_{L1} - \\ + V_{L2} - \\ + V_{L_{eq}} - \\ \hline L_{eq} = L_1 + L_2 \end{array} \right\} \text{same current}$$

$$L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

$$L_{eq} \frac{di}{dt} = (L_1 + L_2) \frac{di}{dt}$$

$$\left. \begin{array}{l} i = i_1 = i_2 \\ \vdots \end{array} \right\} i = i_1 = i_2$$


$$\int \text{both side} \quad \text{Total } E_q \text{ inductance of series circuit is sum of inductance}$$

$$[L_{eq} = L_1 + L_2]$$

$$L_{eq} = L_1 + L_2$$

Circuit is sum of inductances connected in series.

(3) Capacitors in series:

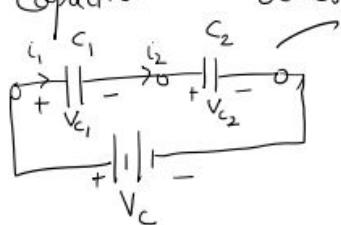

\therefore Series \rightarrow same current flowing.
 $i = i_1 = i_2$


$$C_{eq} = ?$$

$$V_{c_1} = \frac{1}{C_1} \int_{-\infty}^t i_1 dt, \quad V_{c_2} = \frac{1}{C_2} \int_{-\infty}^t i_2 dt$$

$$\frac{1}{C_{eq}} \int_{-\infty}^t i dt = \frac{1}{C_1} \int_{-\infty}^t i dt + \frac{1}{C_2} \int_{-\infty}^t i dt$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \quad \text{or} \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

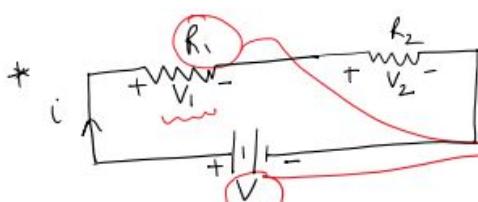or $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n}$ \rightarrow Reciprocal of total Eq. Capacitor of series connection is sum of reciprocal of individual Capacit., connected in series.



$$V_1 = i R_1 \quad V_2 = i R_2$$

Voltage divider rule
in series of R

$$\left\{ R = \frac{1}{G} \right\}$$

By

$$V_2 = V \cdot \frac{R_2}{R_1 + R_2}$$

$$V_1 = V \cdot \frac{R_1}{R_1 + R_2}$$

$$V_1 = V \cdot \frac{G_1}{G_1 + G_2}$$

$$V_2 = V \cdot \frac{G_2}{G_1 + G_2}$$

$$V_1 = V \cdot \frac{G_1}{G_1 + G_2}$$

So

$$\frac{V_1}{V_2} = \frac{R_1}{R_2}$$

OR

$$\frac{V_1}{V_2} = \frac{G_2}{G_1}$$

R \rightarrow resistance

1. Inverse \leftrightarrow 1

$R \rightarrow$ Resistance $G \rightarrow$ Conductance $R = \frac{1}{G}$

 Analysis of Parallel Ckt:-

(1) Resistors in llal:

$$I = I_1 + I_2 + I_3$$


$$V = I_1 R_1$$

$$I_1 = \frac{V}{R_1} , V = I_2 R_2$$

$$I_2 = \frac{V}{R_2}$$

$$V = I_3 R_3$$

$$I_3 = \frac{V}{R_3}$$

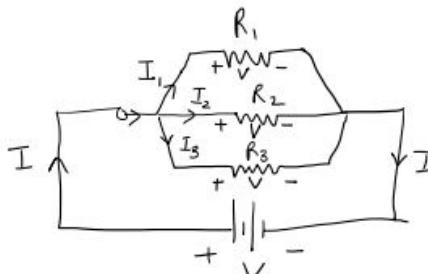

$$I = I_1 + I_2 + I_3 \quad \left\{ \text{In llal current will divide} \right.$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \rightarrow \text{Eq resistance.}$$

$$\text{we know } R = \frac{1}{G} \text{ or } G = \frac{1}{R}$$

$$G_{eq} = G_1 + G_2 + G_3 \rightarrow G = \text{conductance.}$$


* NTF
for $n=2$ $R_1 \neq R_2 \rightarrow$ are in llal

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$$


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\left. \begin{array}{l} R_{eq} < R_1 \\ R_{eq} < R_2 \\ R_{eq} < R_n \end{array} \right\}$$

(2) Inductors in llal:

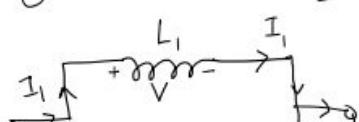


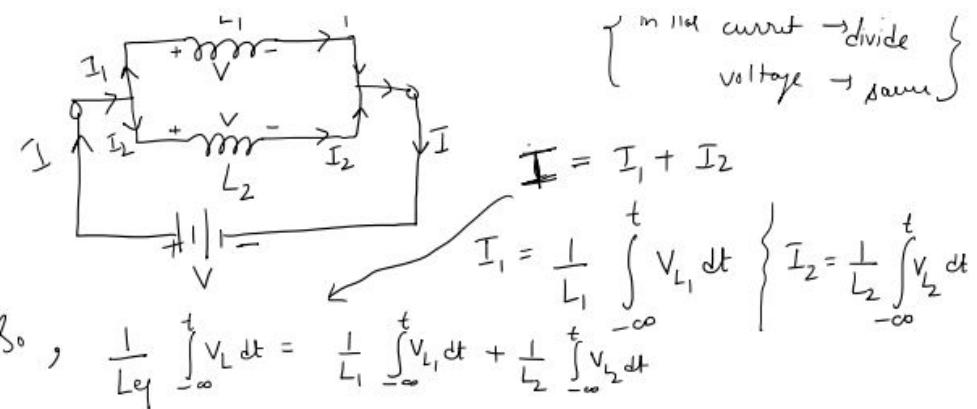
$\left. \begin{array}{l} \text{in llal current } \rightarrow \text{divide} \\ \text{voltage } \rightarrow \text{same} \end{array} \right\}$



Differentiate both sides
 $\frac{I}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$ $\left\{ \begin{array}{l} V_L = V_{L_1} = V_{L_2} = V \\ \because \text{Voltage across 1/Ind} \\ \text{ckt} \rightarrow \text{source} \end{array} \right.$

Or $\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \dots \frac{1}{L_m}$

③ Capacitors in 1/Ind:

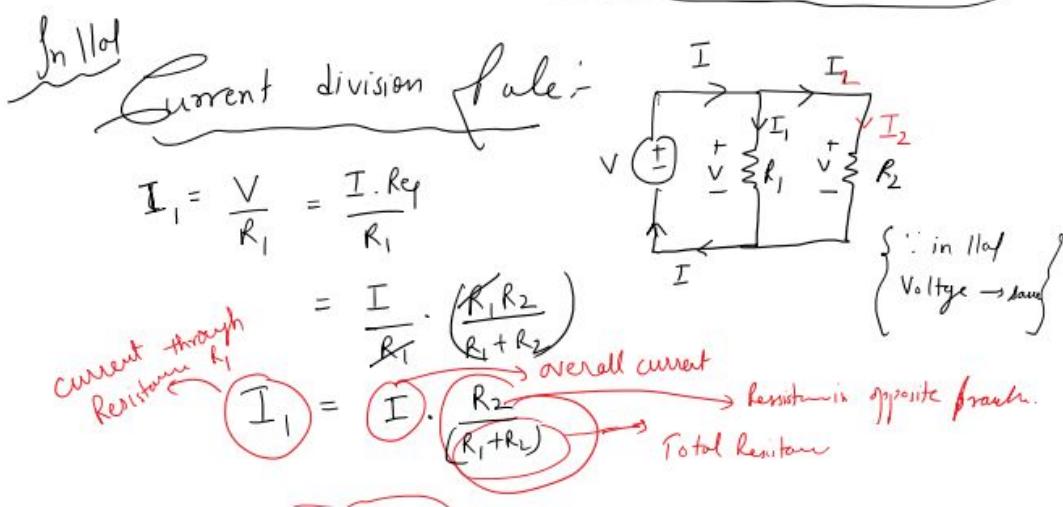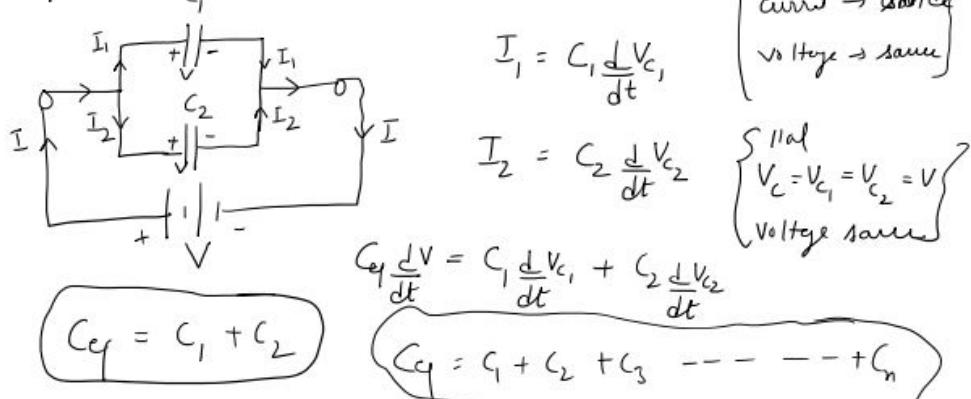



$I_2 = I \cdot \frac{R_1}{R_1 + R_2}$ Current division rule
 In parallel Ckt

Left Series Ckt
 Voltage division rule
 $V_1 = V \cdot \frac{R_1}{R_1 + R_2}$


$V_2 = V \cdot \frac{R_2}{R_1 + R_2}$



by * Current through series combination remain same.
 while
 { Voltage get divided.

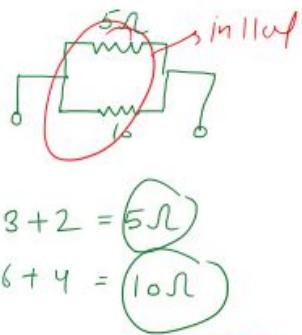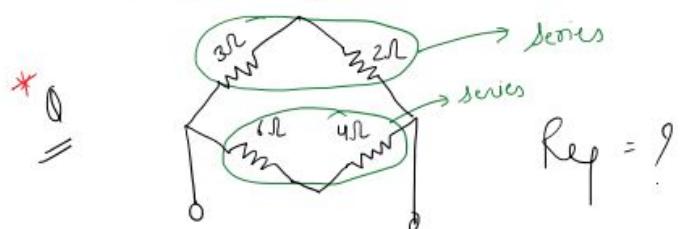Voltage remain same in parallel combination
 { Current get divided.



$$R_{eq} = 5 || 10 = \frac{R_1 R_2}{R_1 + R_2} = \frac{50}{15} = 3.33\Omega$$

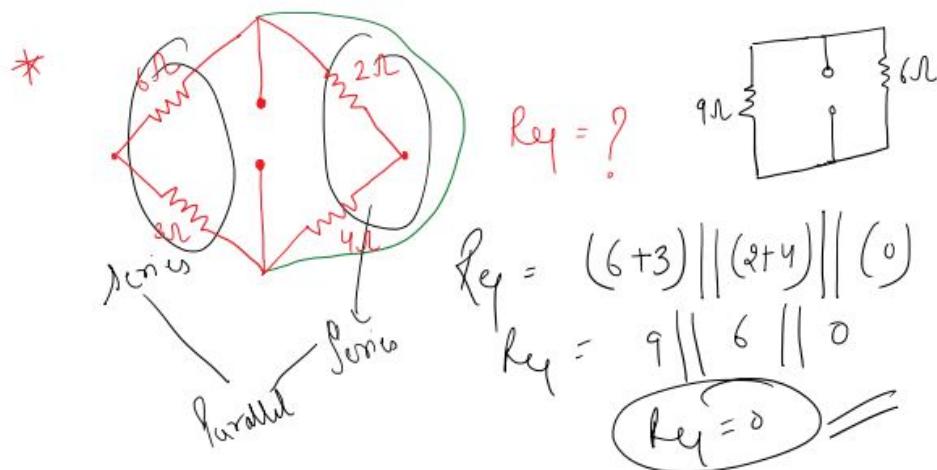

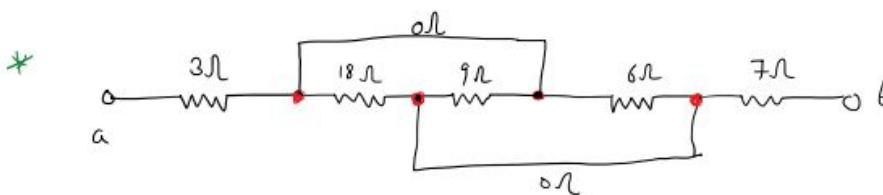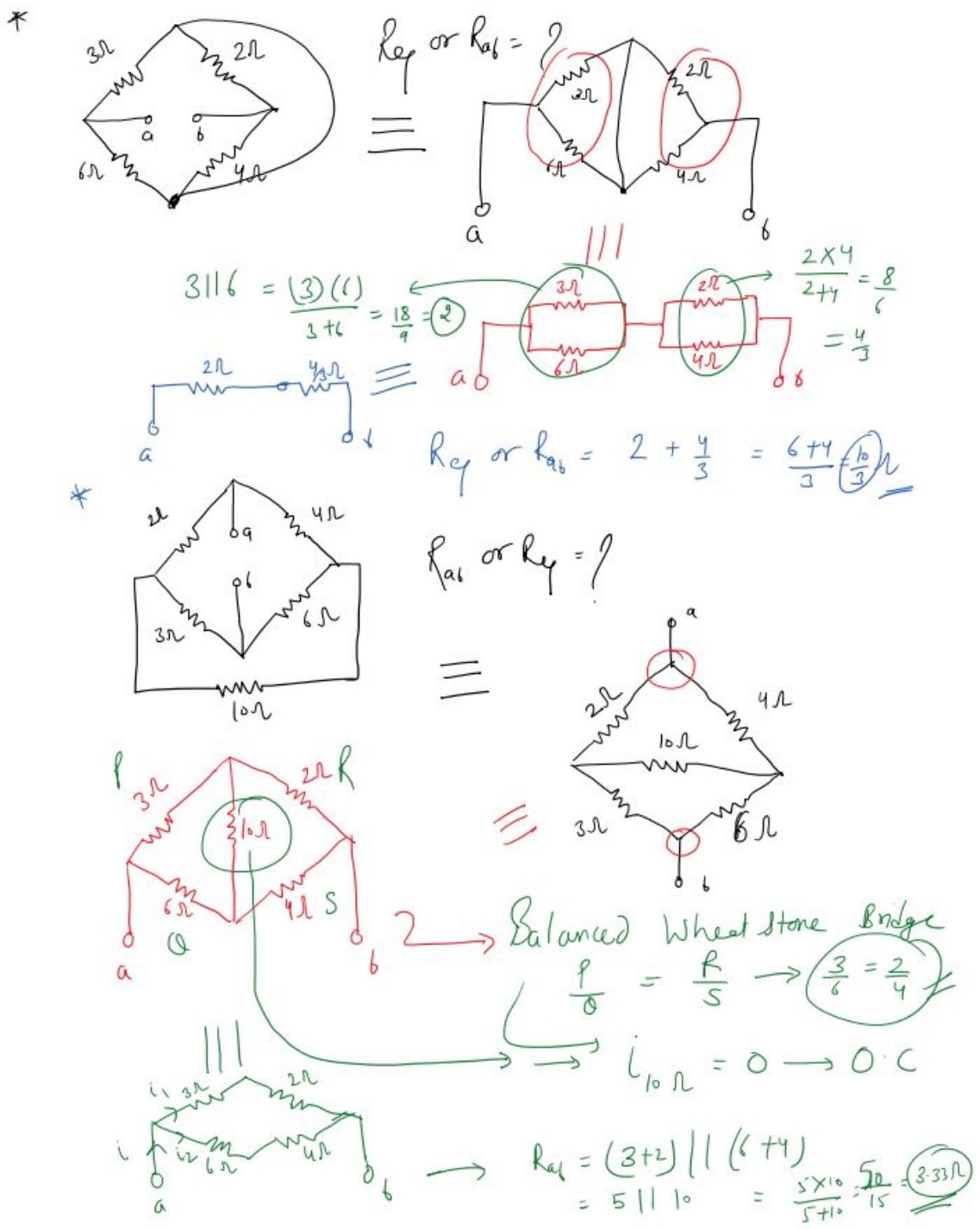


$$R_{ab} = ?$$

$$3\parallel 18\parallel 9$$

$$6\parallel 9\parallel 18$$


$$R_{ab} = ?$$

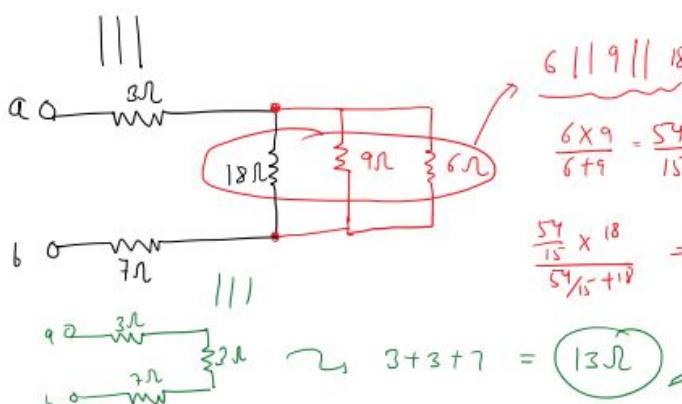

$$\frac{54}{15} \times \frac{18}{54/15 + 18} = 3\Omega$$

$$3 + 3 + 7 = 13\Omega$$

\rightarrow

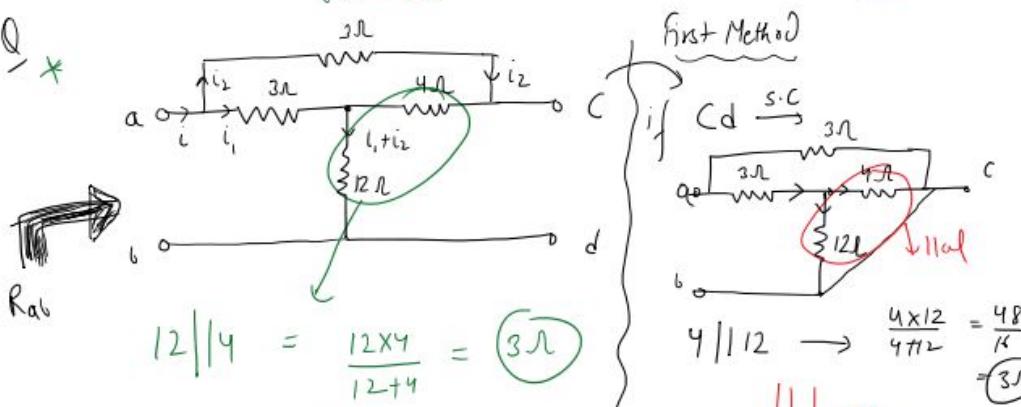


$$12||4 = \frac{12 \times 4}{12+4} = 3\Omega$$


$$3 + 3 = 6\Omega$$

$$6 \parallel 3 = \frac{6 \times 3}{6+3} = \frac{18}{9} = 2\Omega$$


First Method

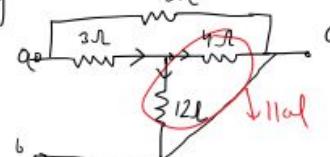

$$4||12 \rightarrow \frac{4 \times 12}{4+12} = \frac{48}{16} = 3\Omega$$

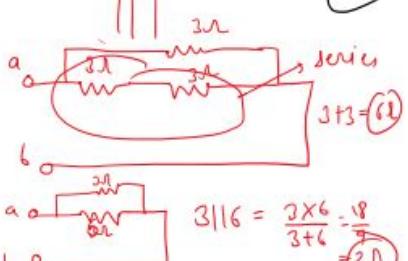

$$3||6 = \frac{3 \times 6}{3+6} = \frac{18}{9} = 2\Omega$$

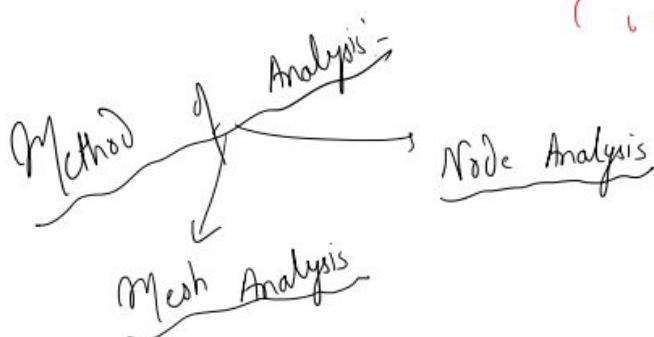

① Mesh Analysis:

Steady state Analysis obtained from


Transient Analysis obtained from

KVL obtained from

Branch Voltage mentioned in



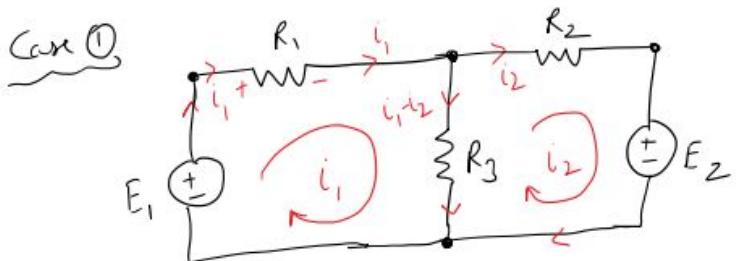
desc.
 Branch
 Current
 in term of
 loop current
 Voltage
 We define mesh as a loop which does not contain any
 other loop with in it.



Step ① Select minimum no. of loops to solve the n/w.
 $l = b - n + 1$ here $b = \text{no. of branches} = 5$
 $n = \text{no. of nodes} = 4$
 $l = 5 - 4 + 1 = 2$

Step ② Express Branch current in terms of loop current & find branch voltage along with polarities.

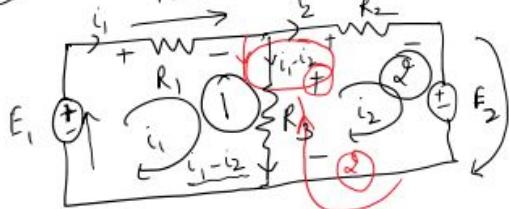Step ③ Apply KVL in each selected loop & solve the eq'




Loop ① KVL $-i_1 R_1 - R_3(i_1 - i_2) + E_1 = 0$

$$-i_1(R_1 + R_3) + i_2 R_3 = -E_1 \quad \boxed{\text{---(1)}}$$

* Loop ② KVL $-i_2 R_2 - E_2 - R_3(i_2 - i_1) = 0$

$$-i_2 R_2 - i_2 R_3 + i_1 R_3 = E_2$$
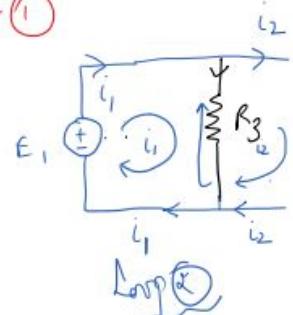
$$-i_2(R_2 + R_3) + i_1 R_3 = E_2 \quad \boxed{\text{---(2)}}$$




$$\begin{bmatrix} -(R_1 + R_3) & R_3 \\ R_3 & -(R_2 + R_3) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -E_1 \\ +E_2 \end{bmatrix}$$

~~Ans~~ ① All diagonal elements will have -ve sign.

② Matrix always satisfy the property of symmetry

$$R_{ij} = R_{ji}$$

Circ 2

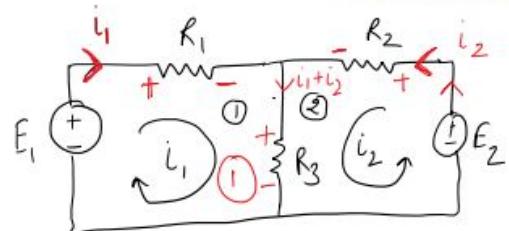

$$\text{Apply KVL in Loop } ① \rightarrow -i_1 R_1 - (i_1 + i_2) R_3 + E_1 = 0 \quad (3)$$

$$\text{Apply KVL in Loop } ② \rightarrow -i_2 R_2 - (i_1 + i_2) R_3 + E_2 = 0 \quad (4)$$

Rewrite eq ③ & ④

$$③ \rightarrow -i_1 R_1 - i_1 R_3 - i_2 R_3 = -E_1 \quad (5)$$



$$\boxed{-i_1 (R_1 + R_3) - i_2 R_3 = -E_1} \quad (A)$$

$$④ \rightarrow -i_2 R_2 - i_1 R_3 - i_2 R_3 = -E_2$$

$$\boxed{-i_1 R_3 - i_2 (R_2 + R_3) = -E_2} \quad (B)$$

$$\begin{bmatrix} -(R_1 + R_3) & -R_3 \\ -R_3 & -(R_2 + R_3) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -E_1 \\ -E_2 \end{bmatrix}$$

Circ 3

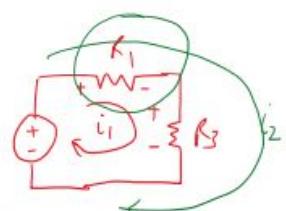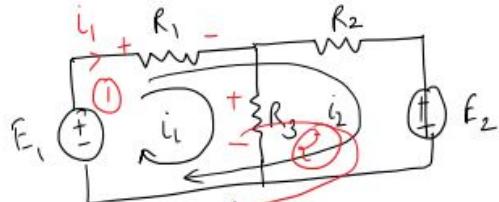


$$\text{Apply KVL in Loop } ① \rightarrow -i_1 R_1 - i_3 R_3 - i_2 R_1 + E_1 = 0$$

Apply KVL in Loop 1 $\rightarrow -i_1 R_1 - i_2 R_3 - E_1 = 0$

$$-i_1(R_1 + R_3) - i_2 R_3 = -E_1 \quad \text{--- (7)}$$

Apply KVL in Loop 2 \rightarrow
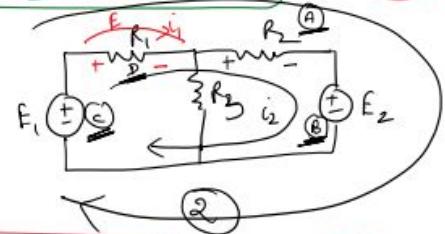
$$-i_2 R_2 - E_2 + E_1 - i_1 R_1 - i_2 R_1 = 0$$




$$-i_2 R_2 - E_2 + E_1 - i_1 R_1 - i_2 R_1 = 0 \quad \text{--- (8)}$$

$$\begin{bmatrix} -(R_1 + R_3) \\ -R_1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -E_1 \\ -E_1 + E_2 \end{bmatrix}$$

If \neq Common resistance in both mesh

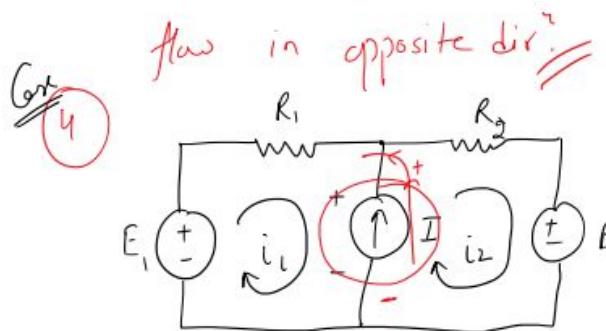
* Take -ve sign if Loop current flow is same direction \nparallel take +ve sign if Loop current



Case 4 when ideal current source comes in one of the loops.

$$I = i_2 - i_1$$

* Super Mesh Analysis :-

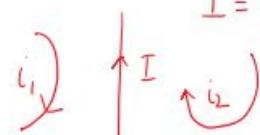


① Express Loop current in terms of current source (I)

$$I = i_2 - i_1$$

② Replace Current source by its internal resistance ie (by open ckt)

which results in super mesh analysis

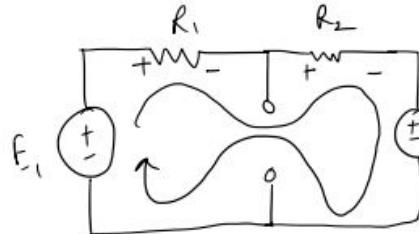


Supermesh

Apply KVL in supermesh by maintaining previous branch voltages.

$$E_1 - i_1 R_1 - i_2 R_2 - E_2 = 0$$

Alternative
→ 2nd prep

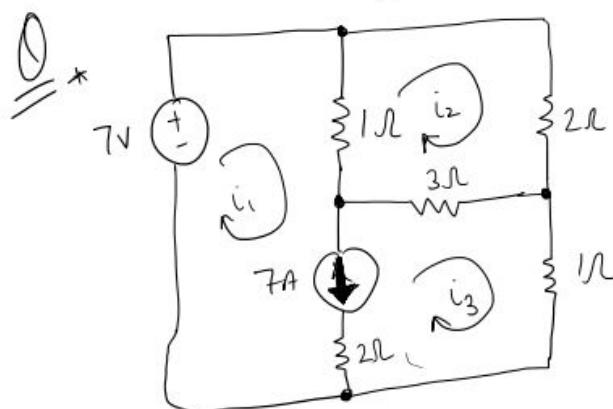Select a loop which doesn't contain current source & apply KVL in it.



$$i_1, i_2 \& i_3 = ?$$

$$l = b - n + 1$$

$$b = 6$$

$$n = 4$$

$$\therefore l = 6 - 4 + 1 = 3$$

* 7A current source is connected along two meshes
mesh ① & mesh ③ ∵ Along these two meshes


a super mesh form.

$$7 = i_1 - i_3 \quad -\textcircled{1}$$



* Apply KVL in supermesh $V = IR$
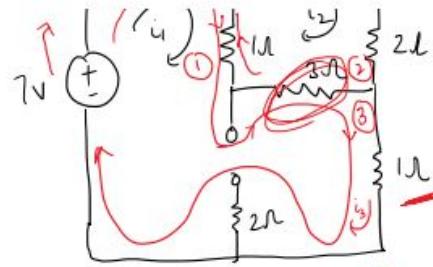
$$- (i_1 - i_3) - 3(i_1 - i_3) - 1(i_1) = 0$$



$$V = IR$$

$$7 - 1(i_1 - i_2) - 3(i_3 - i_2) - 1(i_3) = 0$$

$$i_1 - 4i_2 + 4i_3 = 7 \quad (1)$$

$$\left\{ \begin{array}{l} 3i_2 \\ i_3 \end{array} \right.$$

* Apply KVL in mesh ②

$$-3(i_2 - i_3) - 1(i_2 - i_1) - 2i_2 = 0$$

$$i_1 - 6i_2 + 3i_3 = 0 \quad (3)$$

$$i_1 = i_1 - i_3 \quad (1)$$

Solve eq ①, ② & ③

$$i_1 = 7 + i_3 \quad (1)$$

Put in eq. ② & ③

in eq ②

$$7 + i_3 - 4i_2 + 4i_3 = 0$$

$$-4i_2 + 5i_3 = 0 \quad (4)$$

$$\text{in eq ③} \quad 7 + i_3 - 6i_2 + 3i_3 = 0$$

$$-6i_2 + 4i_3 = -7 \quad (5)$$

Solve eq ④ & ⑤

$$i_2 =$$


$$2.5 \text{ A}$$

$$i_3 =$$

$$2 \text{ A}$$

$$\begin{aligned} i_1 &= 7 + i_3 \\ &= 7 + (2) \\ i_1 &= 9 \text{ A} \end{aligned}$$

∴

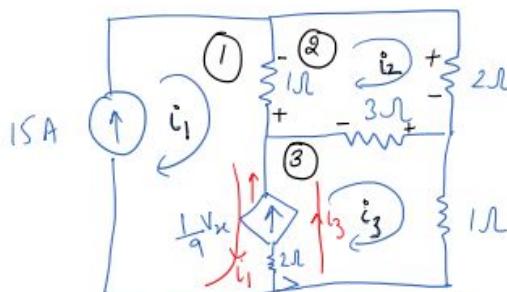

Note
* Presence of two current sources in the 3 mesh ckt makes it necessary to apply KVL only once around mesh ②.

Solution:

$$i_1 = ? \quad i_2 = ? \quad i_3 = ?$$

Apply KVL in mesh ②

Solution

Apply KVL in mesh ②

$$-1(i_2 - i_1) - 2(i_2) - 3(i_2 - i_3) = 0$$

Rewrite

$$+i_1 - 6i_2 + 3i_3 = 0 \quad \text{---} ①$$

loop ①

$$i_1 = 15A \quad \text{---} ② \quad \checkmark$$


through current source $\rightarrow \frac{1}{9}V_x = (i_3 - i_1)$ --- ③

$$* \frac{1}{9}V_x = i_3 - 15$$

$$\therefore i_3 = \frac{1}{9}V_x + 15$$

Put value of i_1 & i_3 in eq ① = ④

Question:

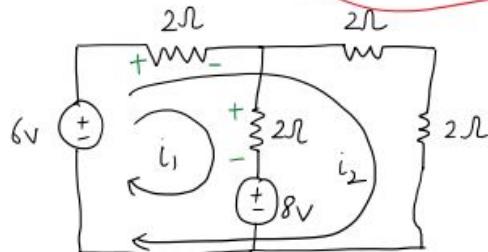

- Find
 a) $i_1 \neq i_2$
 b) V_o

- c) $P_{8V} \neq P_{6V}$
 { S.P. / A.I. }
 S.P. \rightarrow Supply power
 A.I. \rightarrow Absorbing power.

Sol:

Apply KVL in loop ①

$$+6 - 2(i_1 + i_2) - 2i_1 - 8 = 0$$

Rewrite

$$-4i_1 - 2i_2 = 2 \quad \text{---} ①$$

Apply KVL in loop ②

$$6 - 2(i_1 + i_2) - 2i_2 - 2i_1 = 0$$

Rewrite

$$-2i_1 - 6i_2 = -6 \quad \text{---} ②$$

for form $\begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} e \\ f \end{bmatrix}$

$$\begin{bmatrix} -4 & -2 \\ -2 & -6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 2 \\ -6 \end{bmatrix}$$

$$-4i_1 - 2i_2 = 2$$

$$x_2 \rightarrow -8i_1 - 4i_2 = 4$$

$$-2i_1 - 6i_2 = -6$$


$$x_4 \rightarrow -8i_1 - 24i_2 = -24$$

$$\therefore i_2 = 1.4A \rightarrow -4i_1 - 2(1.4) = 2$$

$$\therefore -4i_1 = 2 + 2.8 \Rightarrow i_1 = -\frac{4.8}{4} = -1.2A$$

$$\begin{array}{l} 20i_2 = 28 \rightarrow i_2 = \frac{28}{20} = \frac{14}{10} \\ = \frac{7}{5} = 1.4A \end{array}$$

$$i_1 = -1.2A \quad i_2 = 1.4A$$

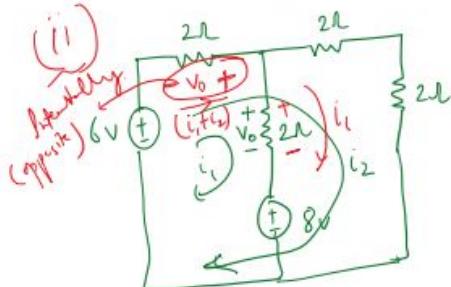

$$V_0 = ? \quad \text{Ohm's Law}$$


$$V_0 = IR$$

$$R = 2\Omega \quad V_0 = 2i_1$$

$$V_0 = -2(i_1 + i_2)$$

$$(ii) P_{8V} = V \times I = 8 \times (-1.2) = -9.6W \quad \text{Absorbing power}$$

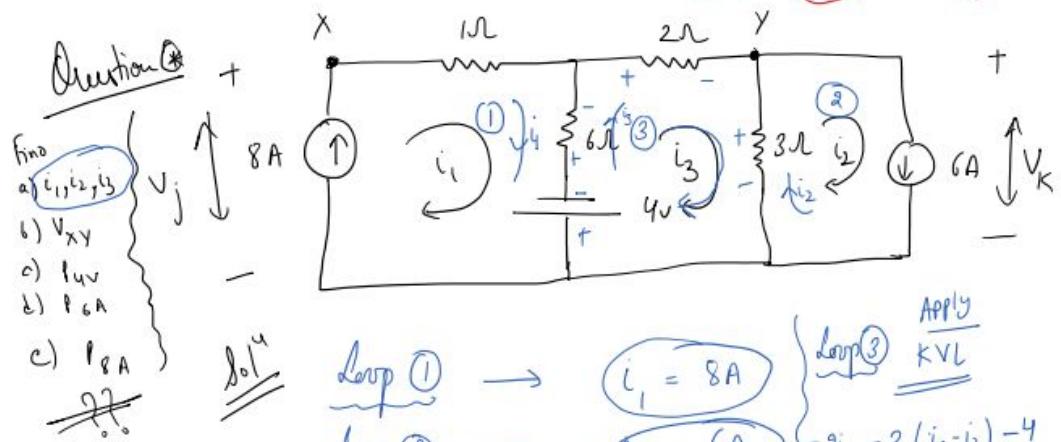
$$(i) P_{6V} = V \times I = 6(i_1 + i_2) = 6(-1.2 + 1.4) = 1.2W \quad \text{Supply power}$$




$$\begin{aligned} \text{Loop 1: } & i_1 = 8A \\ \text{Loop 2: } & i_2 = 6A \\ \text{Loop 3: } & -2i_3 - 3(i_3 - i_2) - 4 \\ & -6(i_3 - i_1) = 0 \\ -2i_3 - 3i_3 + 18 - 4 - 6i_3 + 48 & = 0 \\ -11i_3 + 62 & = 0 \\ i_3 & = +\frac{62}{11} = 5.64A \end{aligned}$$

fronte $-2i_3 - 3(i_3 - 6) - 4$

$-6i_3 + 6(8) = 0$

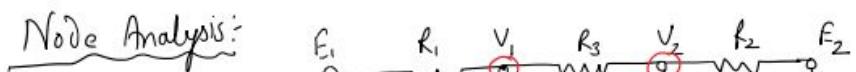

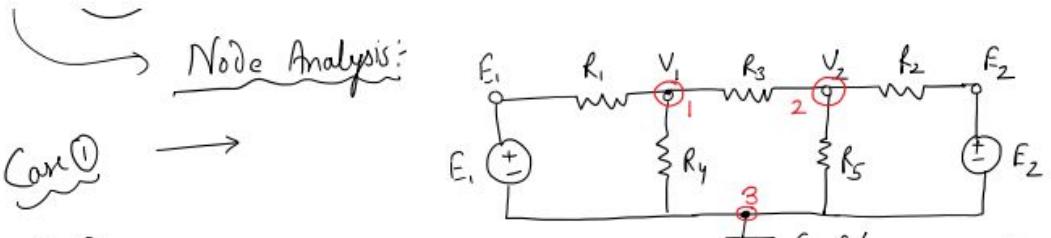


Case ① →

Step ① Determine minimum no. of nodes to solve
the n/w
 $n = 3$ → 1 → ref. node or → {
or datum node
or zero node
→ $n-1 \rightarrow$ non-ref. nodes
(2)

Step ② Express branch voltage in terms of node voltages & also find branch currents along with dir.

Step ③ Apply KCL at each selected (Node 1 & Node 2) non-reference node { solve the eqns }

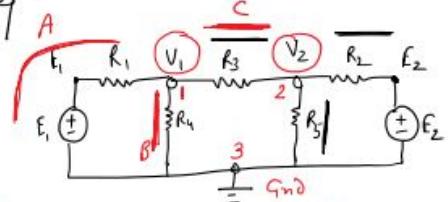Apply KCL at node ①
(Assumption $V_1 > V_2$)



$$\frac{V_1 - E_1}{R_1} + \frac{V_1 - 0}{R_4} + \frac{V_1 - V_2}{R_3} = 0$$

{ Ohm's law $\Rightarrow I = \frac{V}{R}$

Rewrite → $V_1 \left[\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4} \right] - V_2 \left[\frac{1}{R_3} \right] = \frac{E_1}{R_1}$ → ①

Apply KCL at node ② (Assumption $V_2 > V_1$)


$$\frac{V_2 - V_1}{R_3} + \frac{V_2 - 0}{R_5} + \frac{V_2 - E_2}{R_2} = 0$$

Rewrite → $-V_1 \left[\frac{1}{R_3} \right] + V_2 \left[\frac{1}{R_3} + \frac{1}{R_5} + \frac{1}{R_2} \right] = + \frac{E_2}{R_2}$ → ②

In Matrix form


$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_3} \\ -\frac{1}{R_3} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} E_1/R_1 \\ E_2/R_2 \end{bmatrix}$$

* Question ①

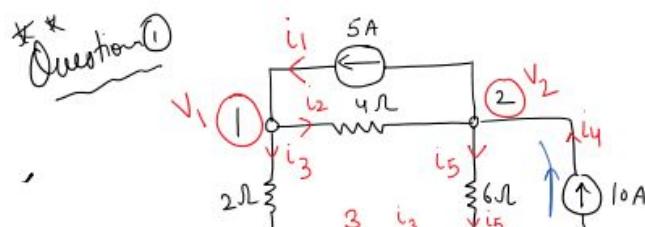

Calculate node voltages in the circuit shown.

Ans: 10V

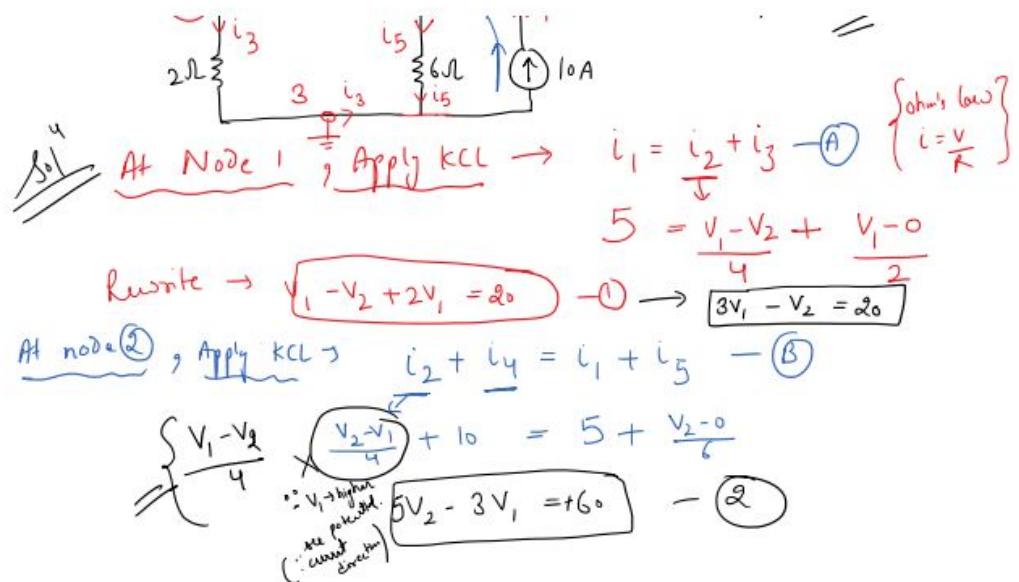

(1) $3V_1 - V_2 = 20$ (2) $-3V_1 + 5V_2 = 60$

(ramer's rule)


$$\begin{bmatrix} 3 & -1 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 60 \end{bmatrix} \quad \begin{cases} V_1 = \frac{\Delta_1}{\Delta} \\ V_2 = \frac{\Delta_2}{\Delta} \end{cases}$$


(D) Determinant $\Delta = \begin{vmatrix} 3 & -1 \\ -3 & 5 \end{vmatrix}_+ = 15 - (-3)(-1) = 15 - 3 = 12$

Calculate value of V_1 & V_2 replace

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 20 & -1 \\ 60 & 5 \end{vmatrix}_+}{12} = \frac{100 - (-60)}{12} = 13.33 \text{ Volt}$$
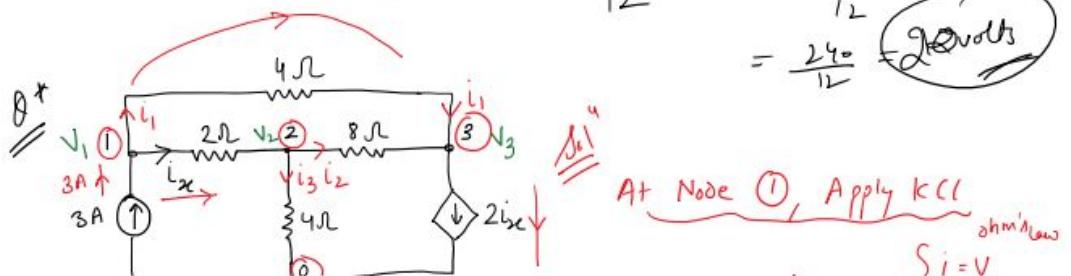
$$V_2 = \frac{\Delta_2}{\Delta} = -\frac{\begin{vmatrix} 3 & 20 \\ -3 & 60 \end{vmatrix}_+}{12} = \frac{180 - (-60)}{12} = \frac{240}{12} = 20 \text{ Volts}$$



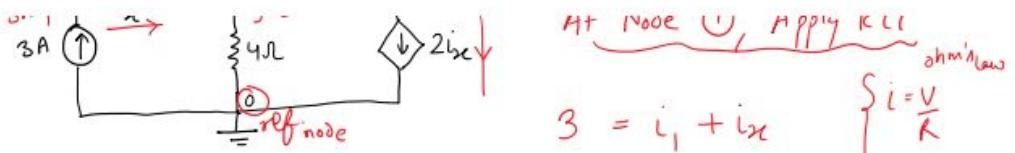

At node ①, Applying KCL ohm's law

$$3 = i_1 + i_2 \quad \left\{ i = \frac{V}{R} \right.$$

$$3 = \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2} \quad \left. \begin{array}{l} \text{shunt law} \\ i = \frac{V}{R} \end{array} \right\}$$

Rewrite → $3V_1 - 2V_2 - V_3 = 12 \quad \text{--- (A)}$

Apply KCL at node ②

$$i_n = i_2 + i_3$$

$$\frac{V_1 - V_2}{2} = \frac{V_2 - V_3}{8} + \frac{V_2 - 0}{4}$$

$$-4V_1 + 7V_2 - V_3 = 0 \quad \text{--- (B)}$$

Apply KCL at node ③

$$i_1 + i_2 = 2i_n \quad \text{outgoing curr.}$$

$$\frac{V_1 - V_3}{4} + \frac{V_2 - V_3}{8} = 2 \left(\frac{V_1 - V_2}{2} \right) \quad \left\{ \begin{array}{l} \text{ohm's law} \\ i = \frac{V}{R} \\ i_n = \frac{V_1 - V_2}{2} \end{array} \right.$$

Rewrite $2V_1 - 3V_2 + V_3 = 0 \quad \text{--- (C)}$

(A) $3V_1 - 2V_2 - V_3 = 12$ } * (row sum rule) $V_1 = \frac{\Delta_1}{\Delta}, V_2 = \frac{\Delta_2}{\Delta}, V_3 = \frac{\Delta_3}{\Delta}$

(B) $-4V_1 + 7V_2 - V_3 = 0$

(C) $2V_1 - 3V_2 + V_3 = 0$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{?}{10}$$

$$\Delta_1 = \begin{vmatrix} 12 & -2 & -1 \\ 0 & 7 & -1 \\ 2 & -3 & 1 \end{vmatrix}$$

{ we repeat first two rows & then cross multiply }

$$\Delta = [21 - 12 + 4 + 14 - 9 - 8] = 10$$

$$\Delta_1 = [84 + 0 + 0 - 0 - 36 - 0] = 48 \quad V_1 = \frac{48}{10}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{?}{10}$$

$$\Delta_2 = \begin{vmatrix} 3 & 12 & -1 \\ -4 & 0 & -1 \\ 2 & 0 & 1 \end{vmatrix} = [0 + 0 + 24 + 0 + 0 + 48]$$

$$V_2 = \frac{-24}{10} = \frac{24}{10} \text{ volts}$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-24}{10} = -2.4 \text{ volts}$$


$$\Delta_3 = \begin{vmatrix} 3 & -2 & 12 \\ -4 & 7 & 0 \\ 2 & -3 & 0 \end{vmatrix} = -24$$

$$\Delta = \begin{vmatrix} 3 & -2 & 12 \\ -4 & 7 & 0 \\ 2 & -3 & 0 \end{vmatrix} = 48$$

$$V_1 = 4.8 \text{ V}$$

$$V_2 = 2.4 \text{ V}$$


$$V_3 = -2.4 \text{ V}$$

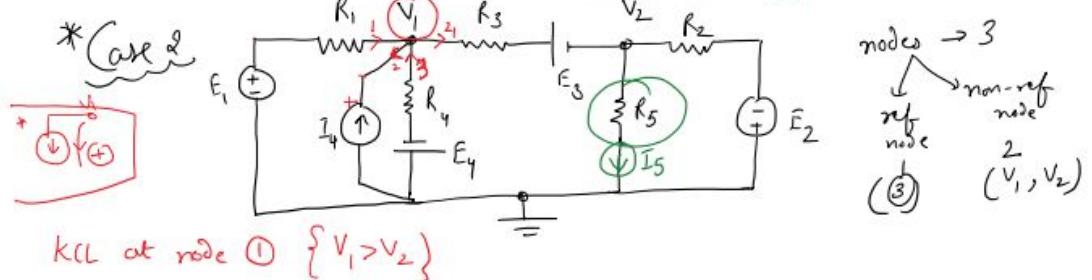

$$\frac{V_1 - E_1}{R_1} - I_4 + \frac{V_1 + E_4}{R_4} + \frac{V_1 - V_2 - E_3}{R_3} = 0$$

Rewrite
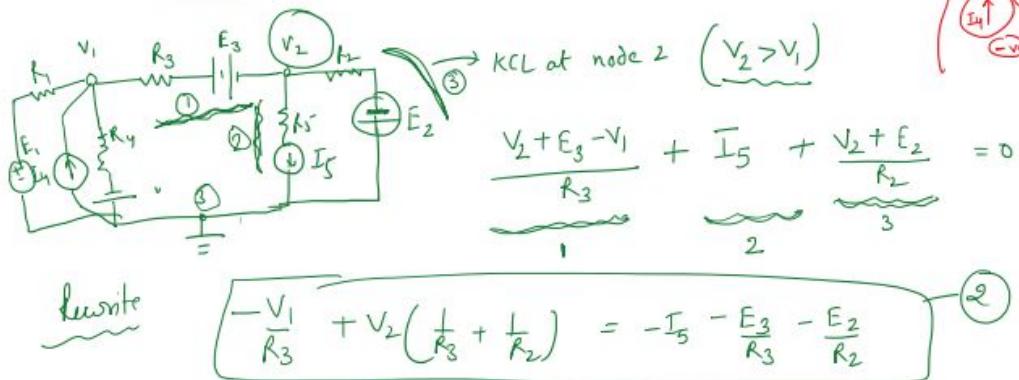
$$V_1 \left[\frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_3} \right] - \frac{V_2}{R_3} = I_4 + \frac{E_1}{R_1} - \frac{E_4}{R_4} + \frac{E_3}{R_3}$$




Rewrite

$$-\frac{V_1}{R_3} + V_2 \left(\frac{1}{R_3} + \frac{1}{R_2} \right) = -I_5 - \frac{E_3}{R_3} - \frac{E_2}{R_2}$$

Matrix form

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_3} & -\frac{1}{R_3} \\ -\frac{1}{R_3} & -\left(\frac{1}{R_2} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{E_1 + I_4 - E_4 + E_3}{R_1} \\ -I_5 - \frac{E_2}{R_2} - \frac{E_3}{R_3} \end{bmatrix}$$

* Case 3

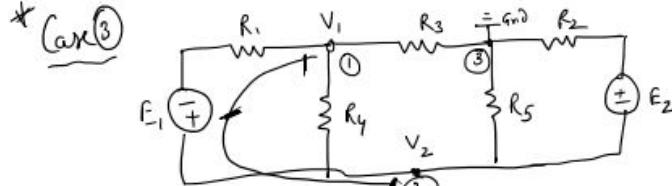

① No. of nodes = 3
1 ref.
2 num-ref
3 non-ref.

Apply KCL at node 1 $(V_1 \text{ is at higher pot})$

$$\frac{V_1 + E_1 - V_2}{R_1} + V_1 - V_2 + \frac{V_1 - 0}{R_2} = 0$$

Rewrite


$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = -E_1$$

$$\begin{aligned} \frac{V_1 + E_1 - V_2}{R_1} + \frac{V_1 - V_2}{R_4} + \frac{V_1 - 0}{R_3} &= 0 \quad \left\{ \begin{array}{l} V_1 \left(\frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_3} \right) - V_2 \left(\frac{1}{R_1} + \frac{1}{R_4} \right) = -E_1 \\ -V_1 \left(\frac{1}{R_1} + \frac{1}{R_4} \right) + V_2 \left(\frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_3} \right) = E_1 - \frac{E_2}{R_2} \end{array} \right. \\ \text{Apply KCL at node ① (Let } V_2 \rightarrow \text{Nodal pt.)} \quad & \text{Rewrite} \end{aligned}$$

$$\frac{V_2 - E_1 - V_1}{R_1} + \frac{V_2 - V_1}{R_4} + \frac{V_2 - 0}{R_5} + \frac{V_2 + E_2}{R_2} = 0$$

Matrix form
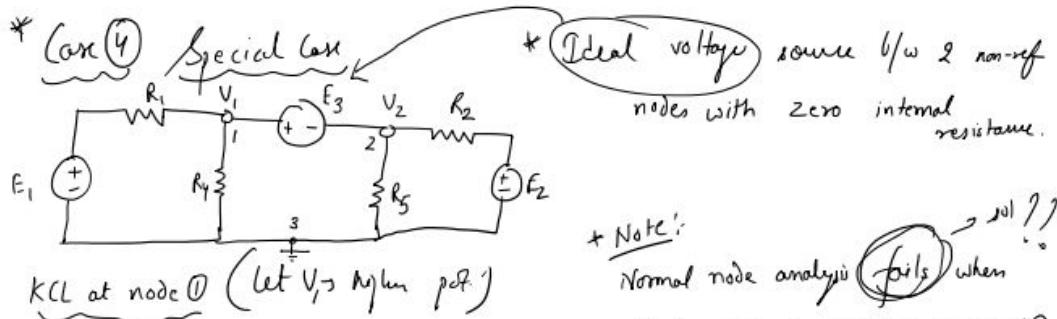
$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_3} & -\left(\frac{1}{R_1} + \frac{1}{R_4}\right) \\ -\left(\frac{1}{R_1} + \frac{1}{R_4}\right) & \left(\frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -\frac{E_1}{R_1} \\ \frac{E_1 - E_2}{R_2} \end{bmatrix} \quad (\text{Ans ③})$$



+ Note:
Normal node analysis fails when ideal voltage source is connected b/w two non-ref. nodes.

Step ① Express node voltage in term of voltage source (E_3)

$$V_1 - V_2 = E_3 \quad ①$$

Step ② Replace volt. source (E_3) by its internal resistance.

{ Int. resistance of ideal voltage source is zero
∴ to replace S.C which leads to supernode




Apply KCL at super node by marking the previous branch current.

method 1 (Supernode)
fails

method 2 (Change ref. node)

or ref. node shifting method.

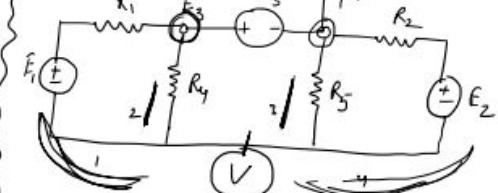

$$\begin{aligned} \frac{V + E_1 - E_3}{R_1} + \frac{V - E_3}{R_4} + \frac{V - 0}{R_5} + \frac{V + E_2 - 0}{R_2} &= 0 \\ V \left[\frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_2} \right] &= -E_1 + E_3 + \frac{E_3}{R_4} - \frac{E_2}{R_2} \quad ① \end{aligned}$$

$$\frac{V_1 - E_1}{R_1} + \frac{V_1 - 0}{R_4} + \frac{V_2 - 0}{R_5} + \frac{V_2 + E_2}{R_2} = 0$$


∴ only 1 eq. is sufficient to solve the ckt.

$$\text{Solve eq. } ① \text{ & } ② \xrightarrow{\text{for } V_1 \text{ & } V_2}$$

Note * There is no restriction in selection of ref. node i.e. any

Solve eq. ① & ② $\xrightarrow{\text{frw}}$ $V_1 \neq V_2$

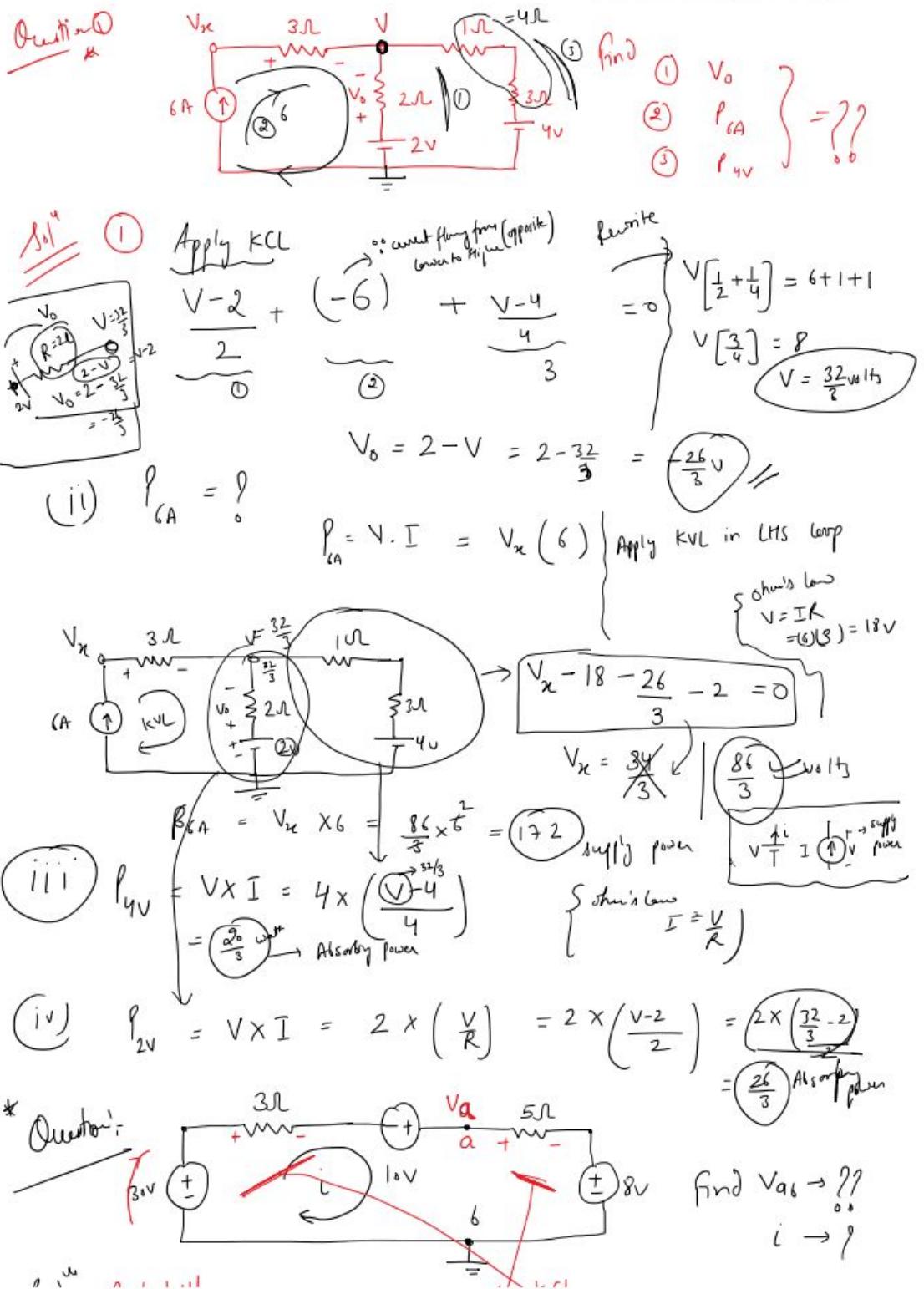Note * There is no restriction in selection of ref. node i.e. any node can be selected as ref. node.



~~Apply KVL~~
 $30 - 3i + 10 - 5i - 8 = 0$
 $40 - 8i - 8 = 0$
 $32 - 8i = 0$
 $i = 4A$

~~Apply KCL at node a~~
 $\frac{V_a - 8}{5} + \frac{V_a - 30 - 10}{3} = 0$
 $V_a \left[\frac{1}{5} + \frac{1}{3} \right] = \frac{8}{5} + \frac{40}{3}$
 $V_a = 28 \text{ Volts}$

$i = \frac{V}{R} = \frac{30 + 10 - 8}{8} = \frac{32}{8} = 4 \text{ Amp}$
 ~~$i = 4 \text{ Amp}$~~
 $4A = \frac{V_a - 8}{5}$
 $V_a = 20 + 8 \Rightarrow V_a = 28 \text{ Volts}$

~~Find $V_1 \neq V_2 = ??$~~
~~Apply KCL at node 1~~
 $-1 + \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{6} = 0$
 $V_1 \left[\frac{1}{2} + \frac{1}{6} \right] - V_2 \left[\frac{1}{6} \right] = 1 \rightarrow \frac{2}{3} V_1 - \frac{V_2}{6} = 1$
 $4V_1 - V_2 = 6$

~~Total nodes $\rightarrow 3$~~
~~1 ref. (3)~~
~~2 non ref. (1, & 2)~~


* Apply KCL at node 2




$$\frac{V_2 - V_1}{6} + \frac{V_2 - 0}{7} + 4 = 0$$

$$-\frac{V_1}{6} + V_2 \left[\frac{1}{7} + \frac{1}{1} \right] + 4 = 0$$

$$7V_1 - 13V_2 = 16$$

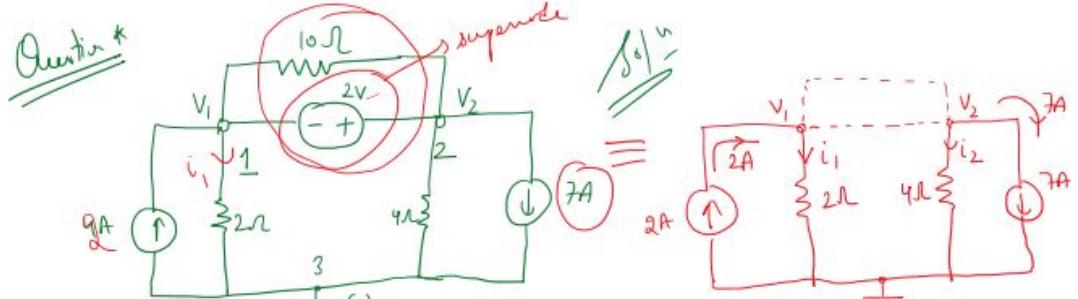Solve eq ① & ②
 $V_1 = -2V$ & $V_2 = -14V$



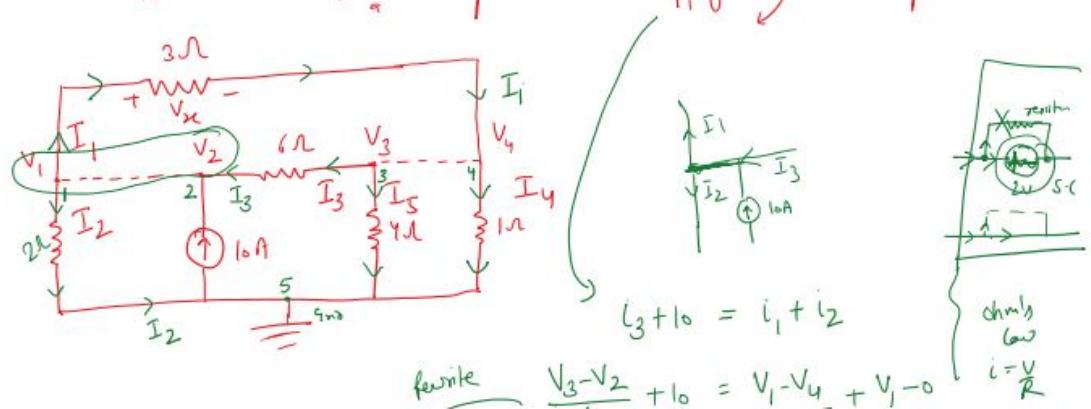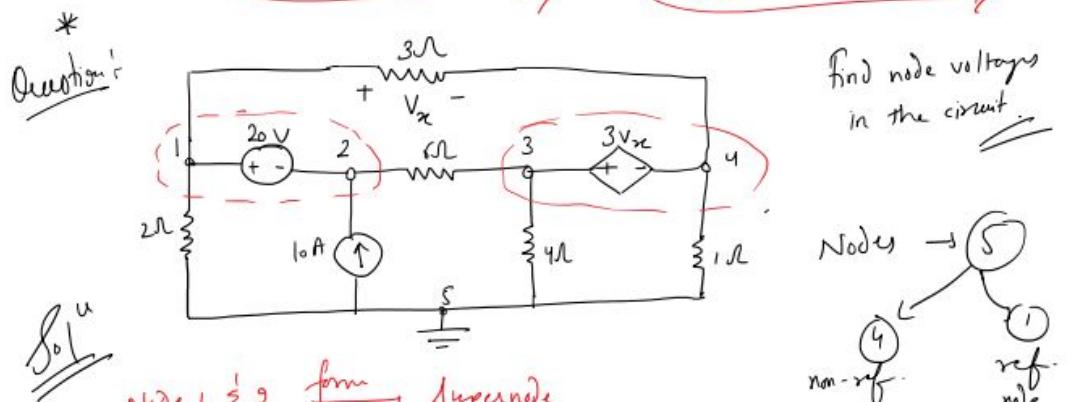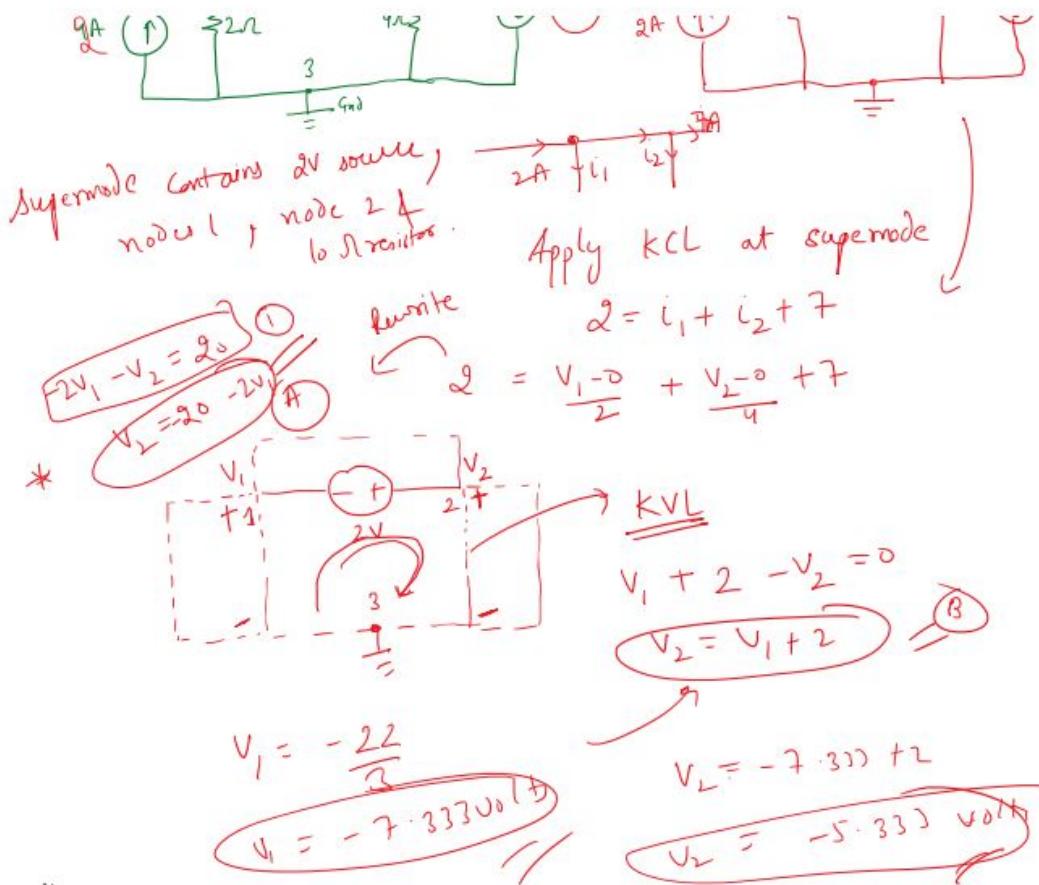

$$I_2 = \frac{V_3 - V_2}{6} + I_0 = \frac{V_1 - V_4}{3} + \frac{V_1 - 0}{2}$$

$I = \frac{V}{R}$


$$5V_1 + V_2 - V_3 - 2V_4 = 60 \quad \boxed{1}$$

Apply KCL at junction ④

$$I_1 = I_3 + I_4 + I_5$$

$$\frac{V_1 - V_4}{3} = \frac{V_3 - V_2}{6} + \frac{V_4 - 0}{1} + \frac{V_3 - 0}{4}$$
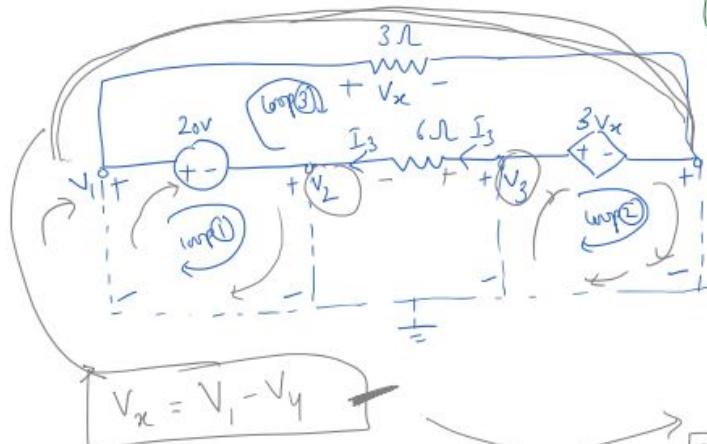
$$4V_1 + 2V_2 - 5V_3 - 16V_4 = 0 \quad \boxed{2}$$



Apply KVL in loop ①

$$V_1 - 20 - V_2 = 0 \quad V_1 - V_2 = 20 \quad \boxed{A}$$

Apply KVL in loop ②

$$V_3 - 3V_x - V_4 = 0$$

$$3V_1 - V_3 - 2V_4 = 0 \quad \boxed{B}$$

Apply KVL in loop ③

$$20 - V_x + 3V_x - 6I_3 = 0 \quad \left\{ \begin{array}{l} \text{As we know } 6I_3 = V_3 - V_2 \\ \text{Rewrite } 6I_3 = V_3 - V_2 \end{array} \right. \quad \boxed{C}$$

$$V_x = V_1 - V_4$$

$$20 - V_1 + V_4 + 3V_1 - 3V_4 - V_3 + V_2 = 0$$

$$2V_1 + V_2 - V_3 - 2V_4 = -20 \quad \boxed{3}$$

from eq. ① $V_2 = V_1 - 20$

$$5V_1 + V_2 - V_3 - 2V_4 = 60 \quad \boxed{1}$$

$$5V_1 + V_1 - 20 - V_3 - 2V_4 = 60$$

$$6V_1 - V_3 - 2V_4 = 80 \quad \boxed{4}$$

$$4V_1 + 2V_2 - 5V_3 - 16V_4 = 0 \quad \boxed{2}$$

1
2
3
4
A
B
C
D
E

Solve eq ④ & ⑤


$$\begin{aligned}
 & \rightarrow (4v_1 + 2v_2 - 5v_3 - 16v_4 = 0) \quad (2) \\
 & 4v_1 + 2v_2 - 40 - 5v_3 - 16v_4 = 0 \\
 & (v_1 - 5v_3 - 16v_4 = 40) \quad (5)
 \end{aligned}
 \left\{
 \begin{array}{l}
 \text{Solve } v_1 \text{ from } (4) \times 5 \\
 \Delta = \begin{vmatrix} 3 & -1 & -2 \\ 6 & -1 & -2 \\ 6 & -5 & -16 \end{vmatrix} = 48 + 60 + 12 - 30 - 96 = 108 - 126 \\
 \Delta = -18
 \end{array}
 \right.$$

$$\Delta_1 = \begin{vmatrix} 0 & -1 & -2 \\ 80 & -1 & -2 \\ 40 & -5 & -16 \end{vmatrix} = 0 + 800 + 80 - 80 - 0 - 1280 \quad \left. \begin{array}{l} \Delta_1 = -480 \\ V_1 = +26.667 \text{ Volts} \end{array} \right\}$$

$$\Delta_2 = \begin{vmatrix} 3 & 0 & -2 \\ 6 & 80 & -2 \\ 6 & 40 & -16 \end{vmatrix} = -3120 \quad \left. \begin{array}{l} V_2 = \frac{\Delta_2}{\Delta} = \frac{-3120}{-18} \\ V_2 = 173.33 \text{ Volts} \end{array} \right\}$$

By $V_2 = -46.667 \text{ Volts}$ $\therefore V_2 = V_1 - 20$

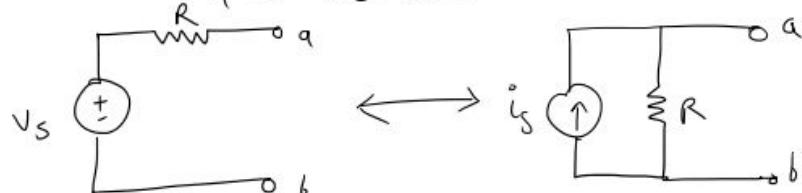* Source Transformation \rightarrow Another tool for simplifying the ckt.
 It is a process of replacing a voltage source V_s in series with a resistor R by a current source i_s in parallel with a resistor R or vice-versa.



(a) Transforming of independent source

* Both ckt & Δ are equivalent provided they have


(a) Transformation of independent source:

- * Both ckt @ & ① are equivalent, provided they have voltage & current relation at terminal a-b.
- * If source are turned off \Rightarrow eq. Resistance $\xrightarrow{\text{in both ckt}}$ 'R'.
- * If terminal a-b short ckt $\frac{\text{S.C.}}{\text{curr}} i_{sc} = \frac{V_s}{R}$ ②

$$i_{sc} = i_s \quad (1)$$

$$\frac{V_s}{R} = i_s$$

* Transformation of dependent source:

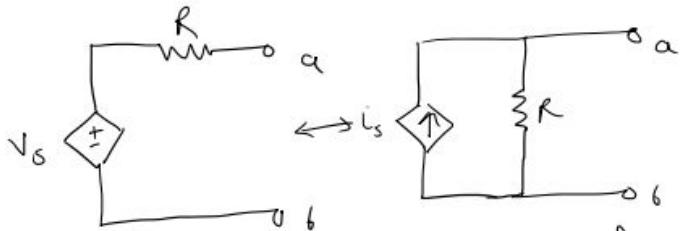


Def
Transformation of dependent source:

- * Note in both figures arrow of current source is directed towards the positive terminal of voltage source.


* Source Transformation $\xrightarrow{\text{is not possible}}$ (i) when $R=0$ {Case of Ideal Voltage source}


(ii) $\xrightarrow{\text{is not possible}}$ when ideal current source with $R=\infty$, can't be replaced. {Practically $R \neq 0$ }
non-ideal Voltage source

Q* Find V_o using source transformation.

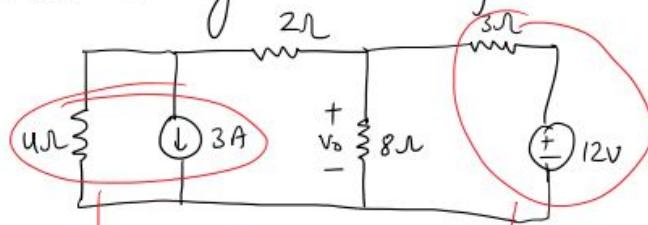

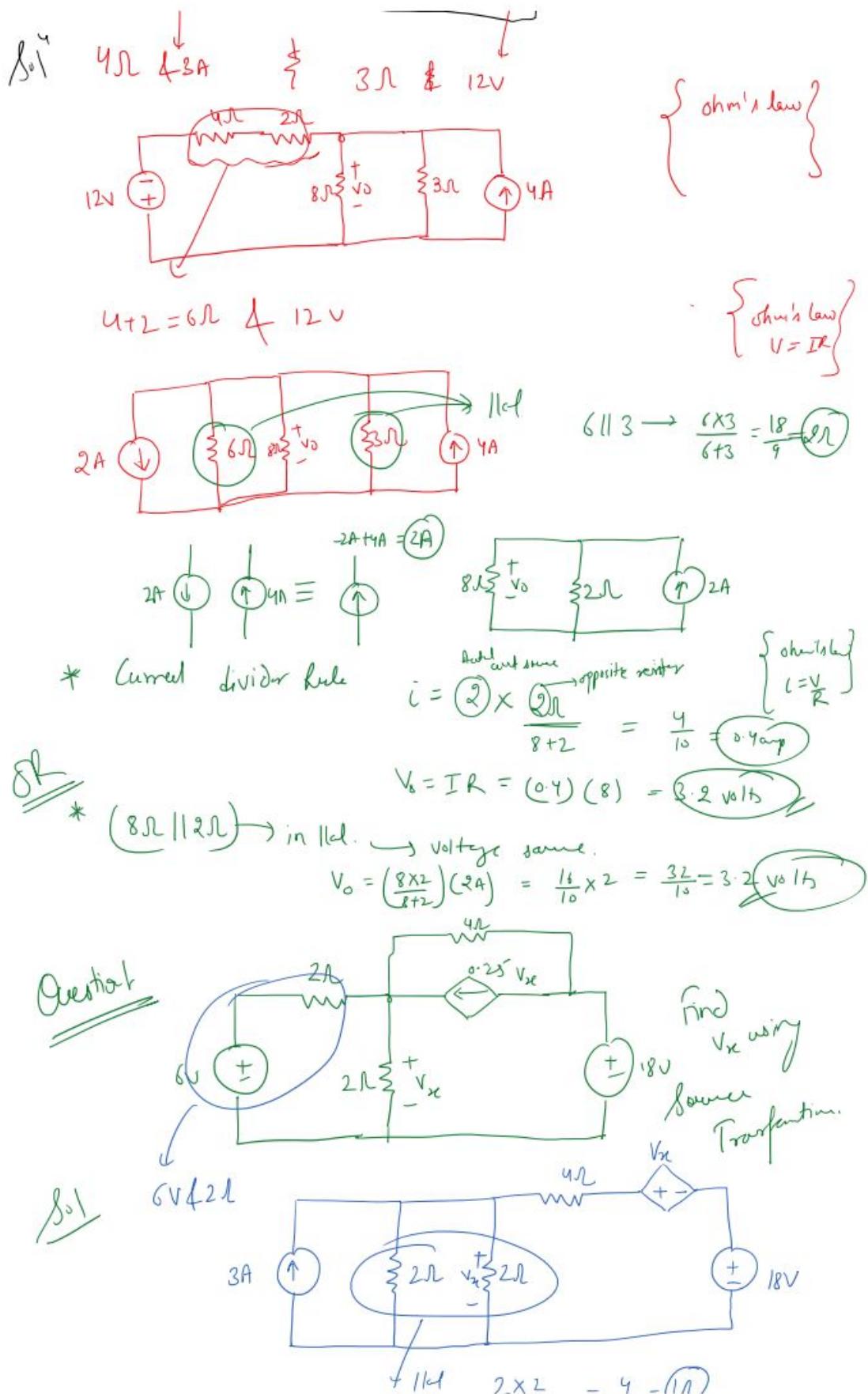
Sol: $4R \parallel 3A$ $\nparallel 8R$ $\nparallel 3R \parallel 12V$



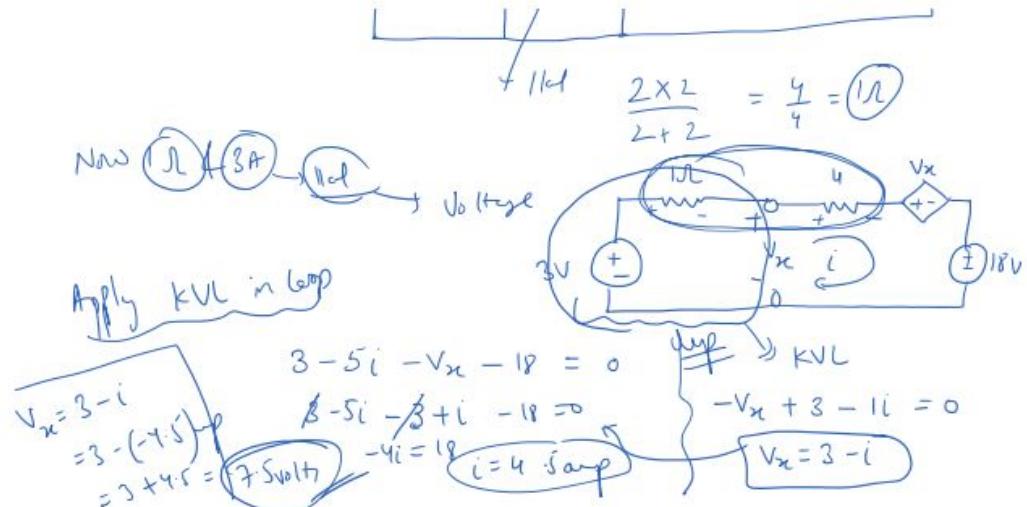

Graph Theory :-

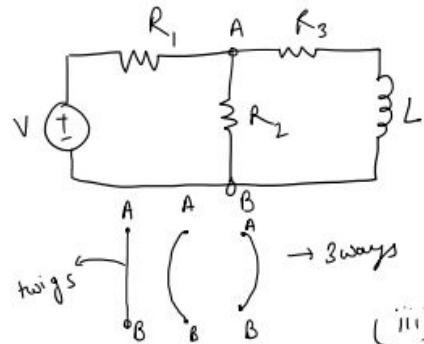Tree :- a set of branches which together connects all the nodes of graphs without forming a loop.




Loop of tree :- ①

(i) All nodes of the graph must be present in the tree.

(ii) Branches of tree (twigs) must be equal to $n-1$. where $n = \text{no. of nodes}$.

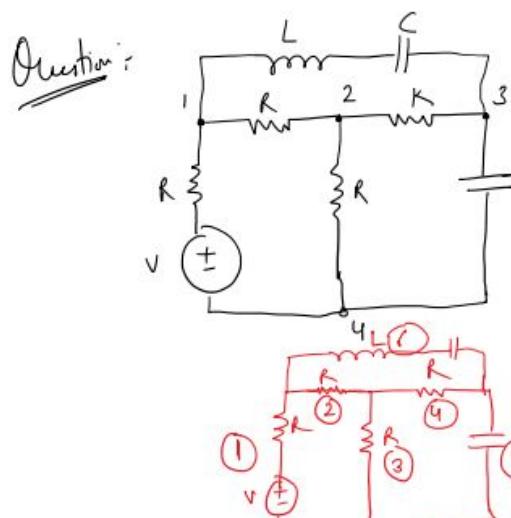(iii) Twigs of tree must be connected in such a manner that no close loop is formed.



Graph → ?

81 branches = 6

Tree → ?

Nodes = $n = 4$


Co-tree → ?


branches = $n-1$
tree (twigs) = 3

nodes →


branches →

→ c branch
graph



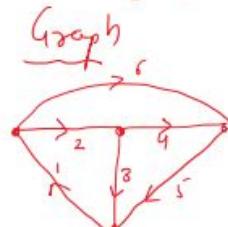


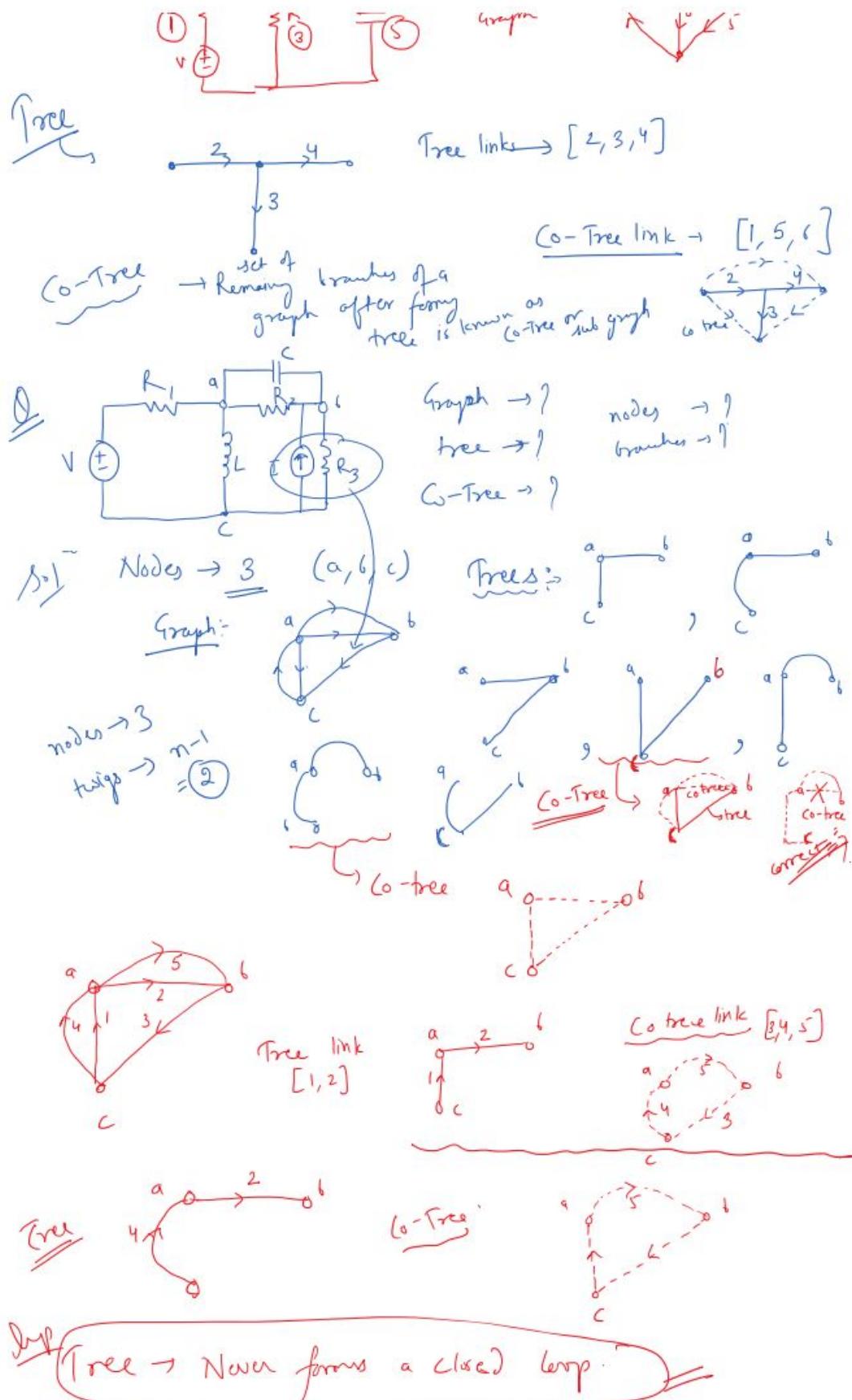

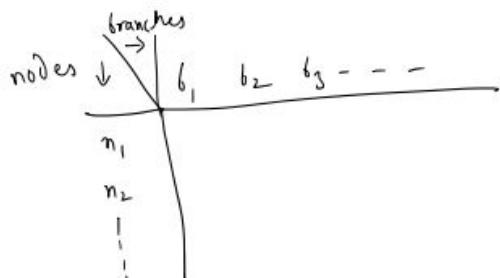
* Incidence Matrix $[A_{ij}]$ → This matrix is drawn w/o



nodes & branches

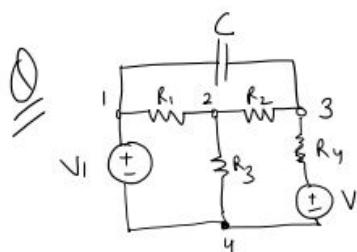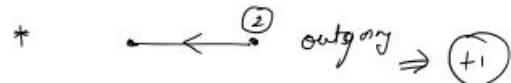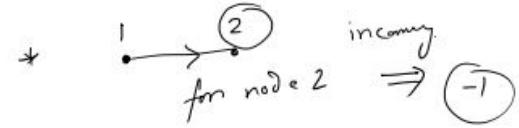

Graph

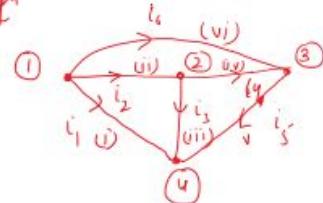

Incidence Matrix

	(i)	(ii)	(iii)	(iv)	(v)	(vi)
1	+1	+1	0	0	0	+1
2	0	-1	+1	+1	0	0
3	0	0	-1	+1	+1	-1
4	-1	0	-1	0	-1	0

Prop of incidence matrix

(i) Sum of entries in any column is zero.

(ii) Determinant of incidence matrix of a linear loop → zero.

(iii) Rank of incidence matrix of connected graph → $n-1$


* Reduced Incidence Matrix: $[A]_{n-1 \times b}$


By eliminating one row from complete incidence matrix.

$$[A] = \begin{bmatrix} +1 & +1 & 0 & 0 & 0 & +1 \\ 0 & -1 & +1 & +1 & 0 & 0 \\ 0 & 0 & 0 & -1 & +1 & -1 \end{bmatrix}$$

* Number of possible tree:

$$\det [A] [A^T]$$


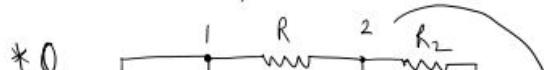


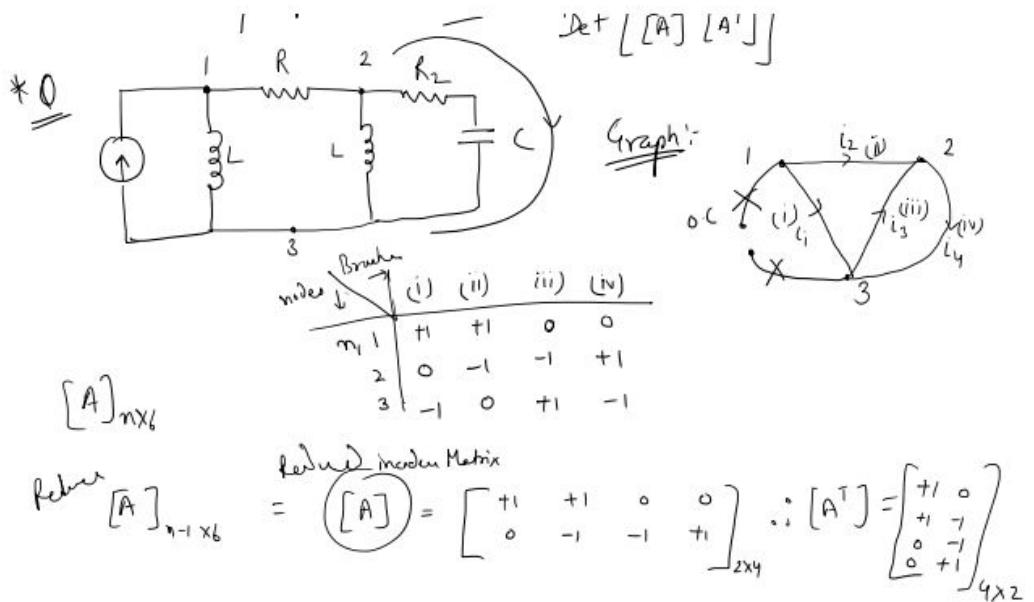

No. of possible trees = $\det [A] [A^T]$

$$= \det \begin{bmatrix} 2 & -1 \\ -1 & 3 \end{bmatrix}_{2 \times 2}$$

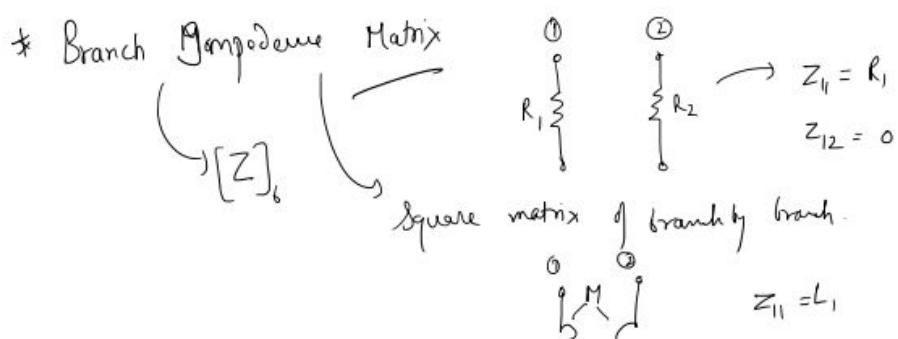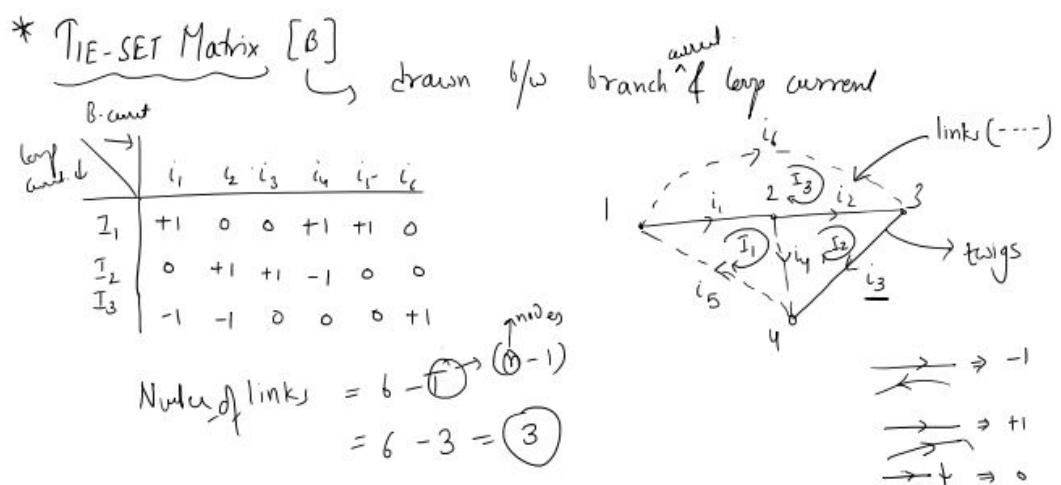Possible trees = $(2 \times 3) - (-1 \times 1) = 6 - 1 = 5$






* Impedance Matrix $[Z] = [B] [Z_b] [B^T]$

$$Z_{11} = L_1$$

$$Z_{22} = L_2$$

$$Z_{12} = M$$

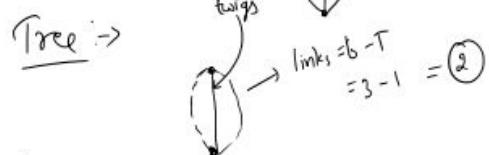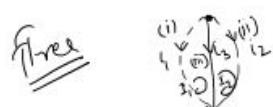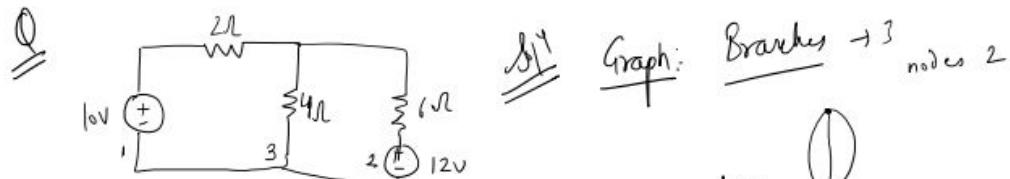


Tie-Set Matrix $(B) \rightarrow$

	i_1	i_2	i_3
i_1	-1	0	+1
i_2	0	+1	-1
i_3			

$$[B] = \begin{bmatrix} -1 & 0 & +1 \\ 0 & +1 & -1 \end{bmatrix} \quad [B^T] = \begin{bmatrix} -1 & 0 \\ 0 & +1 \\ +1 & -1 \end{bmatrix}$$

$$\begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{bmatrix}$$

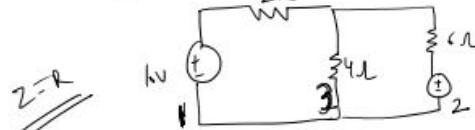Branch Impedance Matrix $\rightarrow [Z_b] = \begin{bmatrix} 2 & 0 & 0 \\ 0 & 6 & 0 \\ 0 & 0 & 4 \end{bmatrix}_{3 \times 3}$




$$[Z] = [B] [Z_b] [B^T]$$

$$= \begin{bmatrix} -1 & 0 & +1 \\ 0 & +1 & -1 \end{bmatrix}_{2 \times 3} \begin{bmatrix} 2 & 0 & 0 \\ 0 & 6 & 0 \\ 0 & 0 & 4 \end{bmatrix}_{3 \times 3} \begin{bmatrix} -1 & 0 \\ 0 & +1 \\ +1 & -1 \end{bmatrix}_{3 \times 2}$$

$$[Z] = \begin{bmatrix} -1 & 0 & +1 \\ 0 & +1 & -1 \end{bmatrix}_{2 \times 3} \begin{bmatrix} -2 & 0 \\ 0 & 6 \\ 4 & -4 \end{bmatrix}_{3 \times 2} = \begin{bmatrix} 6 & -4 \\ -4 & 10 \end{bmatrix}_{2 \times 2}$$

* Equation of KVL : $[Z] [I_b] = [B] \left[[V_s] - [Z_b] [I_s] \right]$

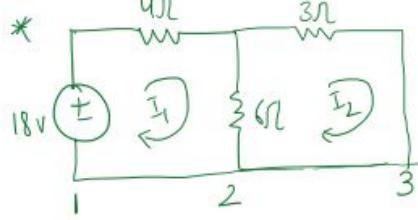* Equation of kVL: $[Z] [I_e] = [B] [V_s] - [Z_b] \overline{[I_s]} \quad //$



find I_1 & I_2 in the ckt
using graph theory


Solⁿ Graph:



Node e → 2

twigs = 1

Tree:

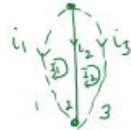

$B = \text{Tree Net Matrix}$

$$\begin{array}{c} \text{branch} \\ \text{tree} \\ \text{net} \end{array} \begin{array}{c} i_1 \\ i_2 \\ i_3 \end{array} \begin{array}{c} i_1 \quad i_2 \quad i_3 \\ \hline I_1 \\ I_2 \end{array} \begin{array}{c} -1 \quad +1 \quad 0 \\ 0 \quad -1 \quad +1 \end{array}$$

$$B = \begin{bmatrix} -1 & +1 & 0 \\ 0 & -1 & +1 \end{bmatrix}_{2 \times 3}$$

$$B^T = \begin{bmatrix} -1 & 0 \\ +1 & -1 \\ 0 & +1 \end{bmatrix}_{3 \times 2}$$

$Z_b = \text{Branch Impedance Matrix}$

$$Z_b = \begin{bmatrix} 4 & 0 & 0 \\ 0 & 6 & 0 \\ 0 & 0 & 3 \end{bmatrix}_{3 \times 3}$$

$$Z = [B] [Z_b] [B^T] = \begin{bmatrix} -1 & +1 & 0 \\ 0 & -1 & +1 \end{bmatrix} \begin{bmatrix} 4 & 0 & 0 \\ 0 & 6 & 0 \\ 0 & 0 & 3 \end{bmatrix} \begin{bmatrix} -1 & 0 \\ +1 & -1 \\ 0 & +1 \end{bmatrix}$$

$$Z = \begin{bmatrix} 10 & -6 \\ -6 & 9 \end{bmatrix}_{2 \times 2} \quad \boxed{-6}$$

Equation of kVL

$$[Z] [I_e] = [B] [V_s] - [Z_b] \overline{[I_s]} \quad \text{source curr not available} \quad \therefore \boxed{\text{X}}$$

$$[Z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 & -6 \\ -6 & 9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -1 & -1 & 0 \\ 0 & -1 & +1 \end{bmatrix} \begin{bmatrix} 18V \\ 0 \\ 0 \end{bmatrix}_{3 \times 1}$$

$$\begin{bmatrix} 10 & -6 \\ -6 & 9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -18 \\ 0 \end{bmatrix}$$

$$\left. \begin{array}{l} 10I_1 - 6I_2 = -18 \\ -6I_1 + 9I_2 = 0 \end{array} \right\} \quad I_1 \neq I_2$$

$$\begin{array}{l} 10I_1 - 36I_2 = -108 \\ + 6I_1 + 9I_2 = 0 \\ \hline 16I_1 = -108 \end{array}$$


$$I_2 = \frac{+108}{64} = -2.1A$$

$$\left\{ \begin{array}{l} 10I_1 - 6(-2) = -18 \\ I_1 = \frac{-30}{12} \\ I_1 = -3A \end{array} \right.$$

$$60I_1 - 36(2) = -10.8 \quad | +72$$

$$60I_1 = 10.8 + 72 \quad | :60$$

$$I_1 = 1.6$$

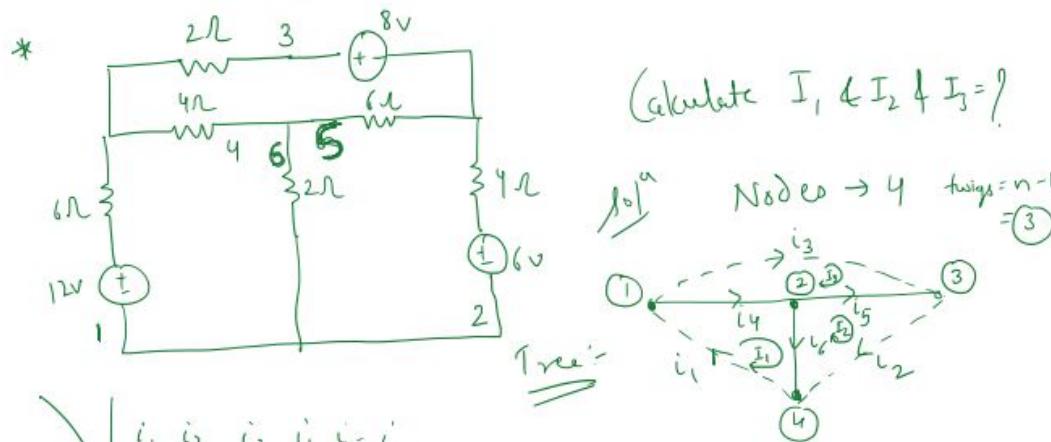

	i_1	i_2	i_3	i_4	i_5	i_6
I_1	1	0	0	1	0	1
I_2	0	+1	0	0	+1	-1
I_3	0	0	+1	-1	-1	0

$$B = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & -1 & 0 \end{bmatrix}_{3 \times 6}$$

$$[Z] = [B] [Z_0] [B^T]$$

$$[Z] = \begin{bmatrix} 12 & -2 & -4 \\ -2 & +12 & -6 \\ -4 & -6 & 12 \end{bmatrix}$$

$$B^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 0 & -1 \\ 0 & +1 & -1 \\ +1 & -1 & 0 \end{bmatrix} \quad 6 \times 3$$

$$= \begin{bmatrix} 6 & 0 & 0 & 0 & 0 \\ 0 & 4 & 0 & 0 & 0 \\ 0 & 0 & 2 & 0 & 0 \\ 0 & 0 & 0 & 4 & 0 \\ 0 & 0 & 0 & 0 & 6 \\ 0 & 0 & 0 & 0 & 2 \end{bmatrix} \quad 6 \times 6$$

$$\left[\begin{array}{ccc} 12 & -2 & -4 \\ -2 & +12 & -6 \\ -4 & -6 & 12 \end{array} \right]_{3 \times 3} \left[\begin{array}{c} I_1 \\ I_2 \\ I_3 \end{array} \right]_{3 \times 1} = \left[\begin{array}{c} 1 \\ 0 \\ 0 \end{array} \right]_{3 \times 1}$$

$$12I_1 - 2I_2 - 4I_3 = 12 \quad \textcircled{1}$$

$$-2\bar{I}_1 + 12\bar{I}_2 - 4\bar{I}_3 = \{ -2$$



$$-4I_1 - 6I_2 + 12I_3 = 8$$

$$\begin{bmatrix} 12 \\ 6 \\ 8 \end{bmatrix}_{3 \times 1}$$

* Cut-set Matrix: $[Q] \rightarrow$ Drawn w.r.t branch voltage & cut-set voltage.


* No. of cut-set = No. of twigs

* Cut-set never cut two twigs.

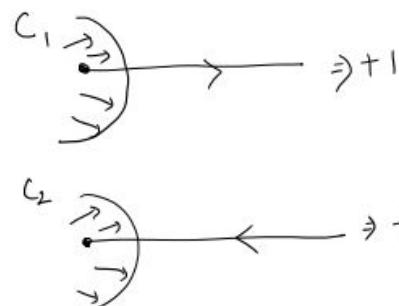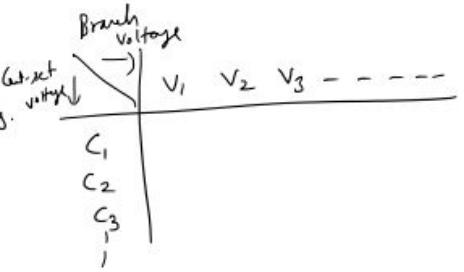


$$- \Rightarrow 0$$

eg:
Tree:

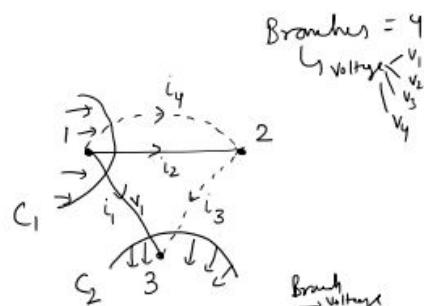


$$\begin{aligned} \text{Nodes} &= 3 = n \\ \text{Twigs} &= n-1 = 3-1 = 2 \end{aligned}$$
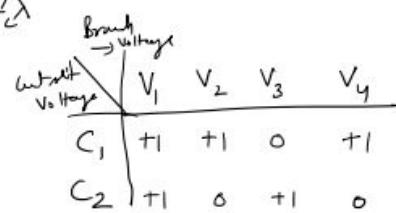
$$\begin{aligned} \text{No. of cut-set} &= \text{No. of twigs} \\ &= 2 \end{aligned}$$




$$O = \begin{bmatrix} +1 & +1 & 0 & +1 \\ +1 & 0 & +1 & 0 \end{bmatrix}$$

eg:
Tree

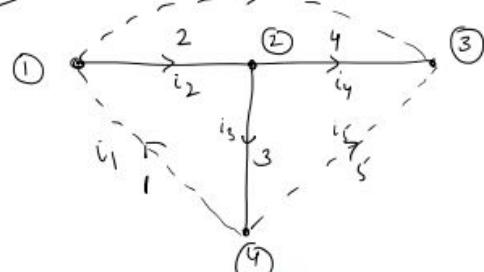

$$\begin{aligned} \text{Branch} &= 6 \\ \text{nodes} &= 4 \end{aligned}$$
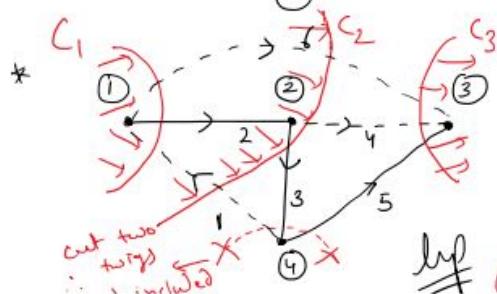
$$\begin{aligned} \text{twigs} &= 3 \\ \text{cut-set} &= 3 \end{aligned}$$




$$\begin{aligned} \text{Branch} &= 6 \\ \text{nodes} &= 4 \\ \text{twigs} &= 3 = \text{Cut-set} \end{aligned}$$

Cut-set never cut two twigs

~~cut two twigs~~ ~~not included~~ ~~(4)~~ ~~leaf~~ Cut-set never cut two twigs

	v_1	v_2	v_3	v_4	v_5	v_6
C_1	-1	+1	0	0	0	+1
C_2	-1	0	+1	+1	0	+1
C_3	0	0	0	+1	+1	+1

* Branch Admittance Matrix :- (y_b)

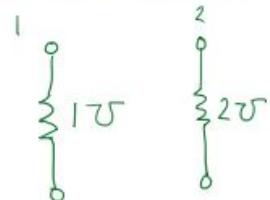

$$y_b = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}_{2 \times 2} = \begin{bmatrix} 1 & 0 \\ 0 & 2 \end{bmatrix}$$

$$y_b = \begin{bmatrix} \frac{1}{2s} & \frac{1}{3s} \\ \frac{1}{5s} & \frac{1}{3s} \end{bmatrix}$$


* Admittance Matrix :- $[Y]$

$$[Y] = \underbrace{\begin{bmatrix} 0 \end{bmatrix}}_{\text{cut-set}} \underbrace{\begin{bmatrix} y_b \end{bmatrix}}_{\text{Branch Admittance Matrix}} \underbrace{\begin{bmatrix} 0^T \end{bmatrix}}_{\text{cut-set Transpose}}$$

* Equation of KCL :-

$$\text{KVL} \rightarrow [Z] [I_L] = [\beta] [V_S] - [z_b] [I_S]$$
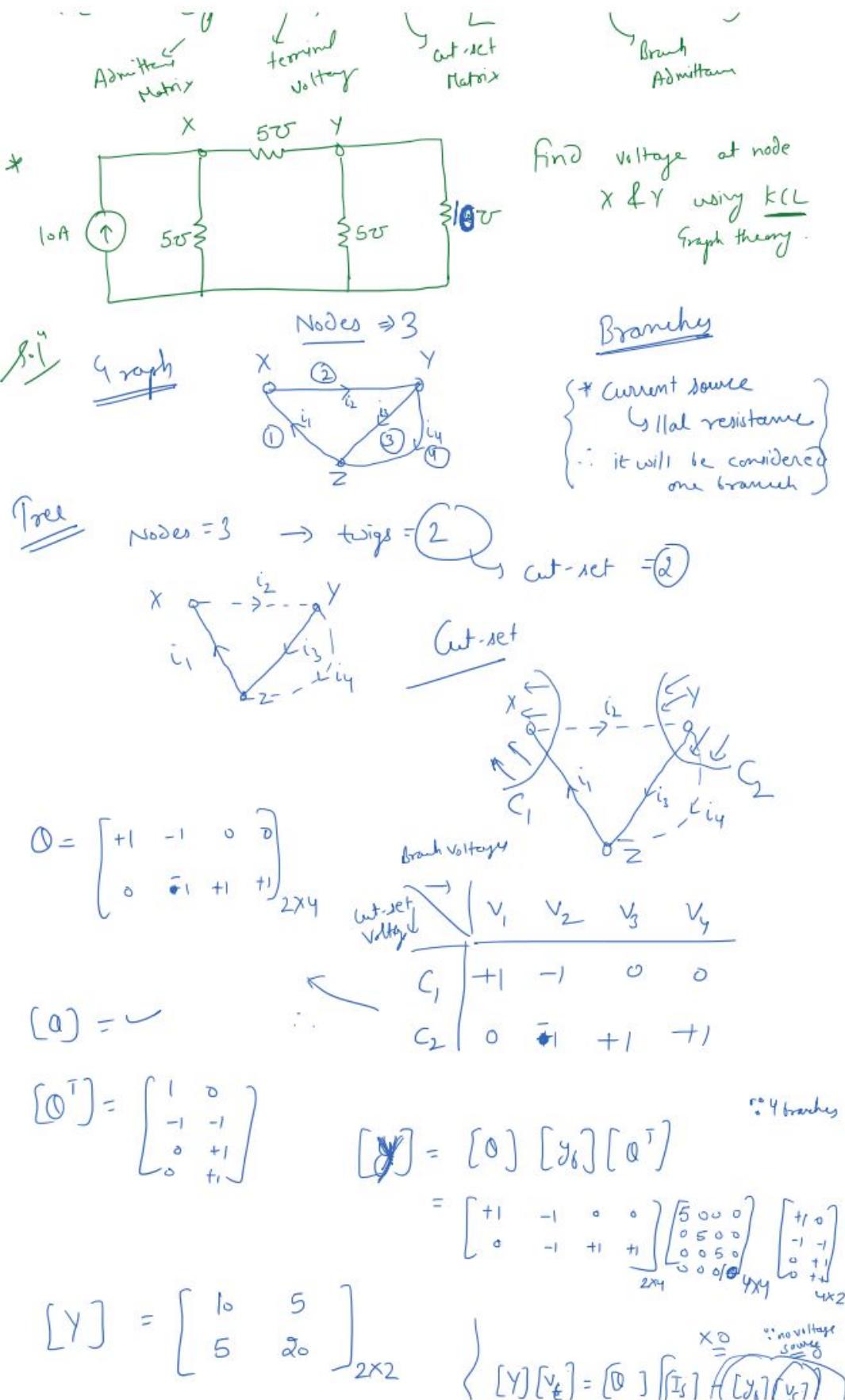
$$\text{KCL} \rightarrow [Y] [V_t] = \underbrace{\begin{bmatrix} 0 \end{bmatrix}}_{\text{Admittance matrix}} \underbrace{\left[\begin{bmatrix} I_S \end{bmatrix} - [Y] [V_S] \right]}_{\text{cut-set matrix}} \underbrace{\begin{bmatrix} V_t \end{bmatrix}}_{\text{terminal vector}}$$



$$L' \cup \left[\begin{matrix} 5 & 20 \\ 1 & 5 \\ 5 & 20 \end{matrix} \right]_{2 \times 2}$$

$$[I_s] = \begin{bmatrix} -10 \\ 0 \\ 0 \\ 0 \end{bmatrix}_{4 \times 1} \quad [V_s] = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}_{4 \times 1}$$

$$\left\{ \begin{array}{l} [Y][V_t] = [0] [I_s] + [y][V_s] \\ \left[\begin{matrix} 1 & -1 & 0 & 0 \\ 0 & -1 & 1 & 1 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{matrix} \right] \left[\begin{matrix} V_x \\ V_y \\ V_z \\ V_t \end{matrix} \right] = \left[\begin{matrix} -10 \\ 0 \\ 0 \\ 0 \end{matrix} \right] \end{array} \right.$$

X0
NO VITIATION
SOURCES

OR

$$\left[\begin{matrix} 0 & 5 \\ 5 & 20 \end{matrix} \right] \left[\begin{matrix} V_x \\ V_y \end{matrix} \right] = \left[\begin{matrix} -10 \\ 0 \end{matrix} \right] \left[\begin{matrix} V_z \\ V_t \end{matrix} \right]_{2 \times 2}$$


$$\left[\begin{matrix} V_x \\ V_y \end{matrix} \right] = \left[\begin{matrix} -10 \\ 0 \end{matrix} \right] \left[\begin{matrix} 20 & 5 \\ -5 & -10 \end{matrix} \right]^{-1}$$

$$\begin{aligned} 10V_x + 5V_y &= -10 \quad \text{Eq. ①} \\ 5V_x + 20V_y &= 0 \quad \text{Eq. ②} \\ V_x &\perp V_y \end{aligned}$$


$V_x = -8/7$


$V_y = 2/7$

* Concept of duality


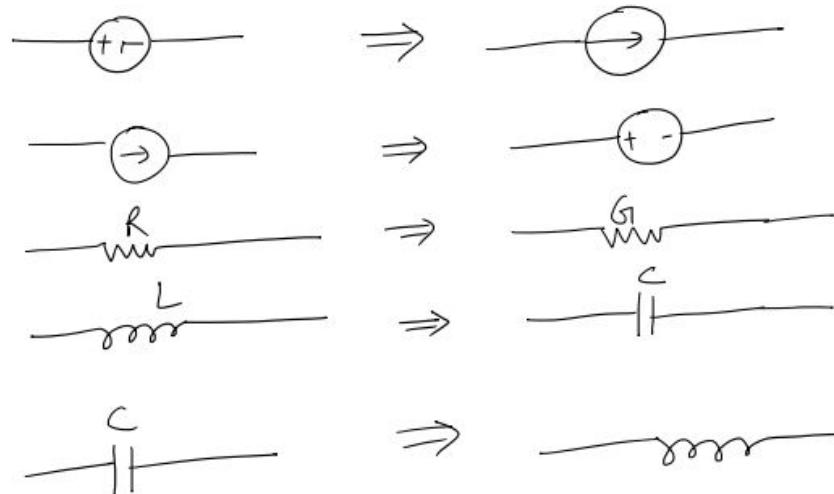


Dual ckt for the Given by :-



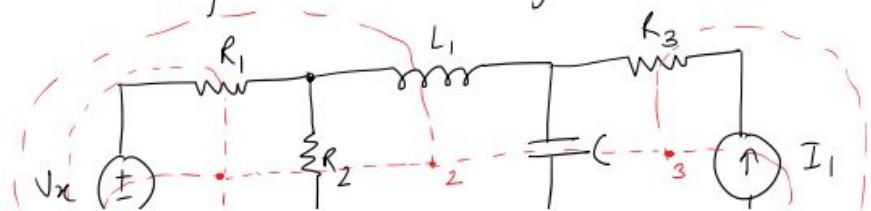


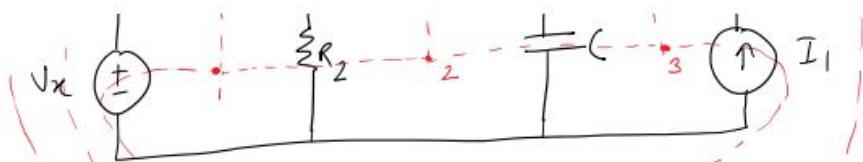

Q1

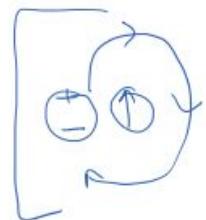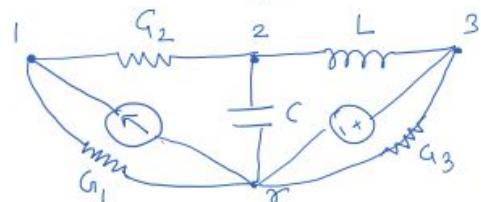




* Q1 Draw dual network of the given ckt.


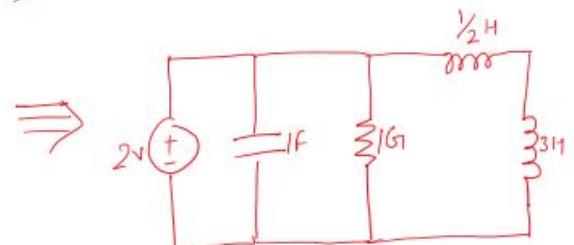
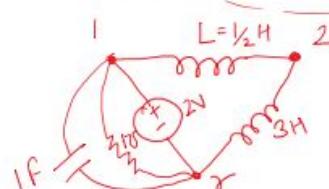
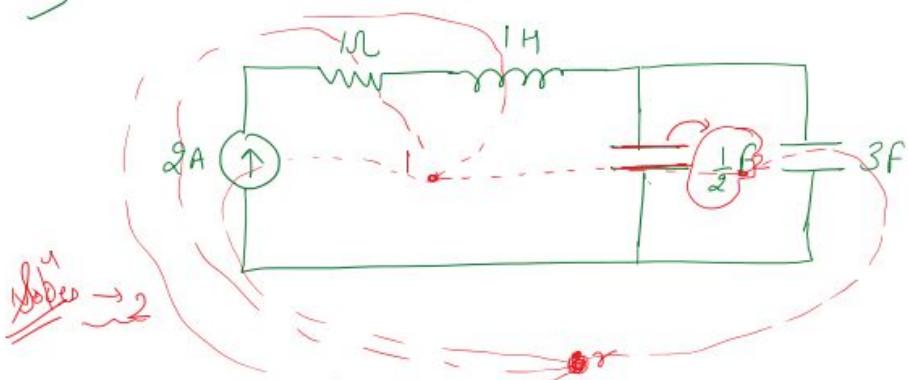


* Q1 Draw dual N/w


Q1
Nodes \rightarrow 4
3nm-ref
1-ref

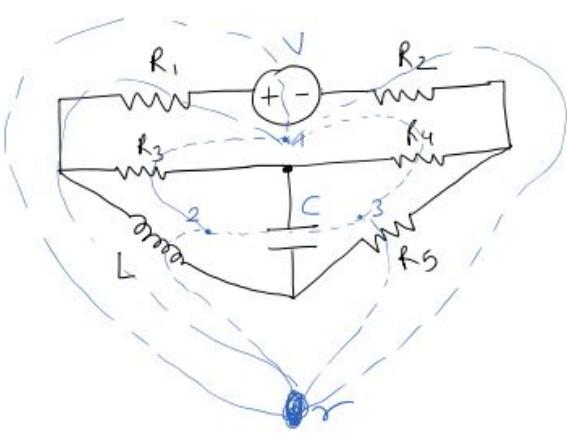

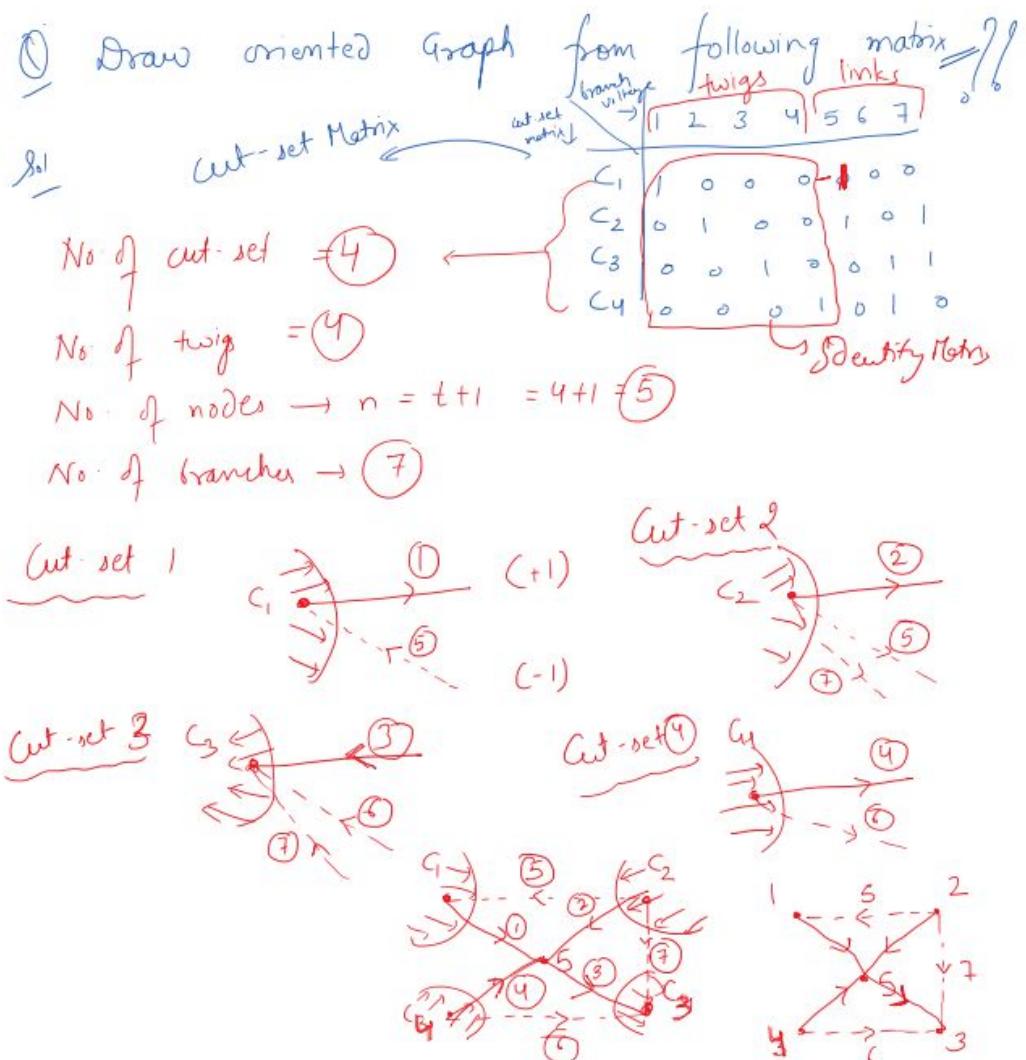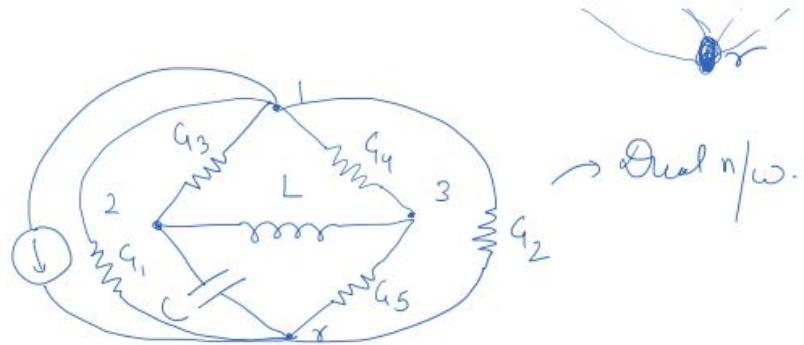

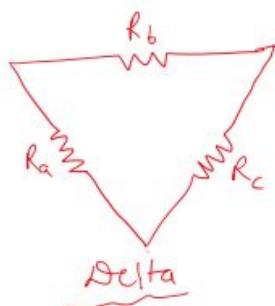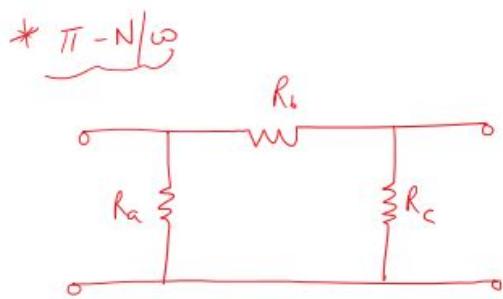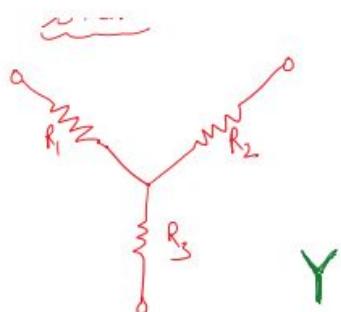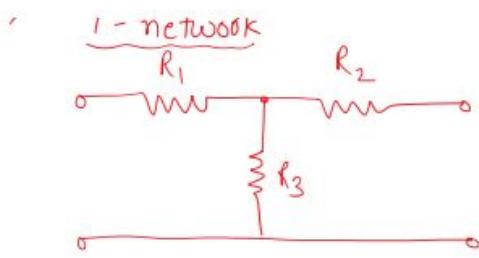

* Delta to star

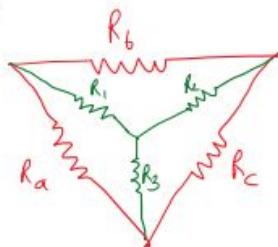

Delta to star


$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$

Star to Delta
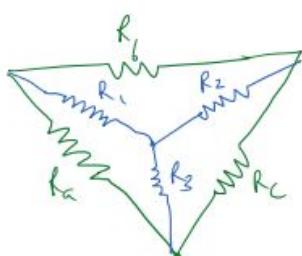
$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$



$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


$$\therefore R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

* Procedure of transformation either from Delta to star

or star to delta $\xrightarrow{\text{for resistors \& inductors}}$

Impedances $\xrightarrow{\text{is}} \text{same.}$

* if \rightarrow

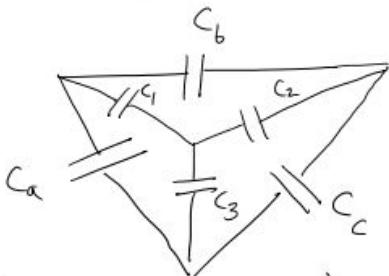

(Y) Star to Σ Delta (Δ)

$$\frac{1}{C_A} = \frac{1}{C_1 C_2} + \frac{1}{C_2 C_3} + \frac{1}{C_3 C_1}$$

$$\frac{1}{C_1} = \frac{\frac{1}{C_1 C_2} + \frac{1}{C_2 C_3} + \frac{1}{C_3 C_1}}{\frac{1}{C_2}}$$

$$\frac{1}{C_2} = \frac{\frac{1}{C_1 C_2} + \frac{1}{C_2 C_3} + \frac{1}{C_3 C_1}}{\frac{1}{C_3}}$$

$$\frac{1}{C_3} = \frac{\frac{1}{C_1 C_2} + \frac{1}{C_2 C_3} + \frac{1}{C_3 C_1}}{\frac{1}{C_1}}$$

Delta to Σ Star

$$\frac{1}{C_1} = \frac{1}{C_A} \cdot \frac{1}{C_6}$$



$$\frac{1}{C_2} = \frac{1}{C_A} + \frac{1}{C_1} + \frac{1}{C_C}$$

$$\frac{1}{C_3} = \frac{1}{C_1} \cdot \frac{1}{C_C}$$

$$\frac{1}{C_3} = \frac{\frac{1}{C_A} \cdot \frac{1}{C_C}}{\frac{1}{C_A} + \frac{1}{C_1} + \frac{1}{C_C}}$$


$$R_{eq} = ??$$

* Q

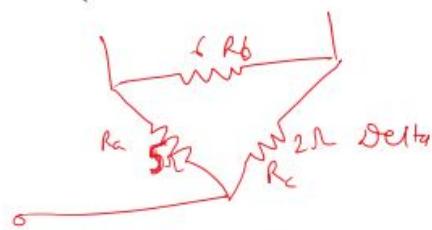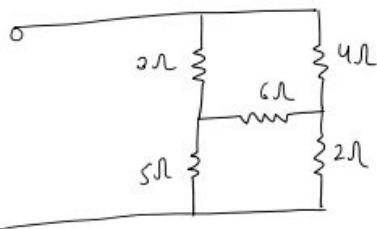


Q)

Delta to Star \Rightarrow

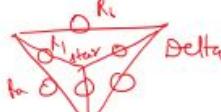


Star




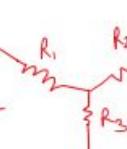




$$R_1 = \frac{6 \cdot 5}{6 + 5 + 2} = \frac{30}{13}$$

$$R_2 = \frac{6 \cdot 2}{6 + 5 + 2} = \frac{12}{13}$$
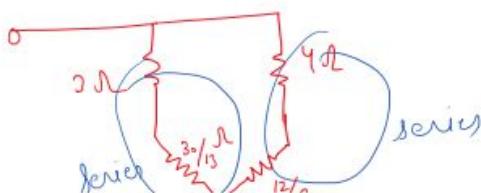
$$\& R_3 = \frac{(5)(2)}{6 + 5 + 2} = \frac{10}{13}$$




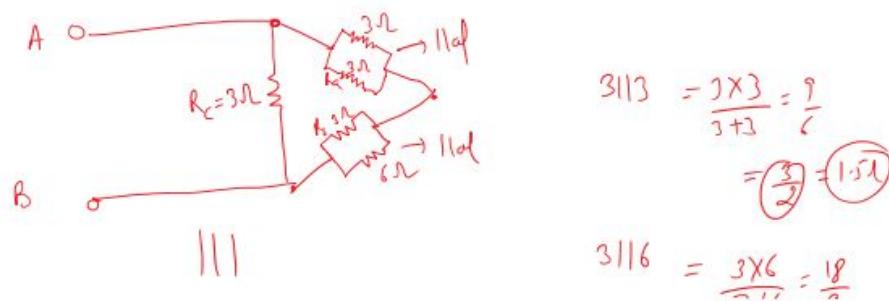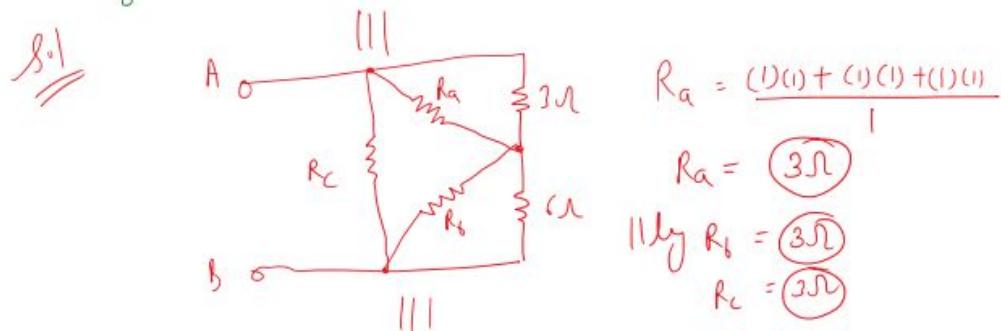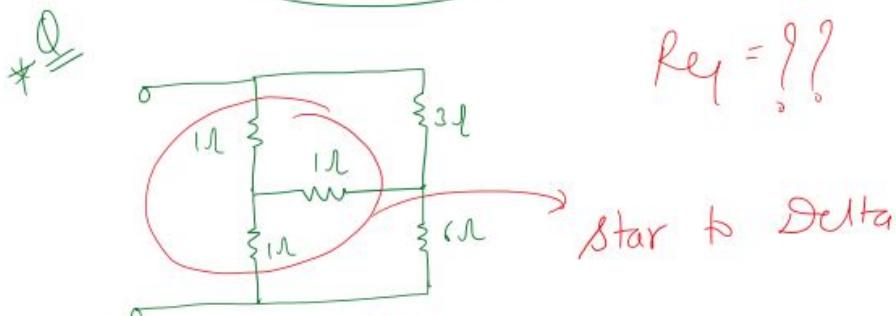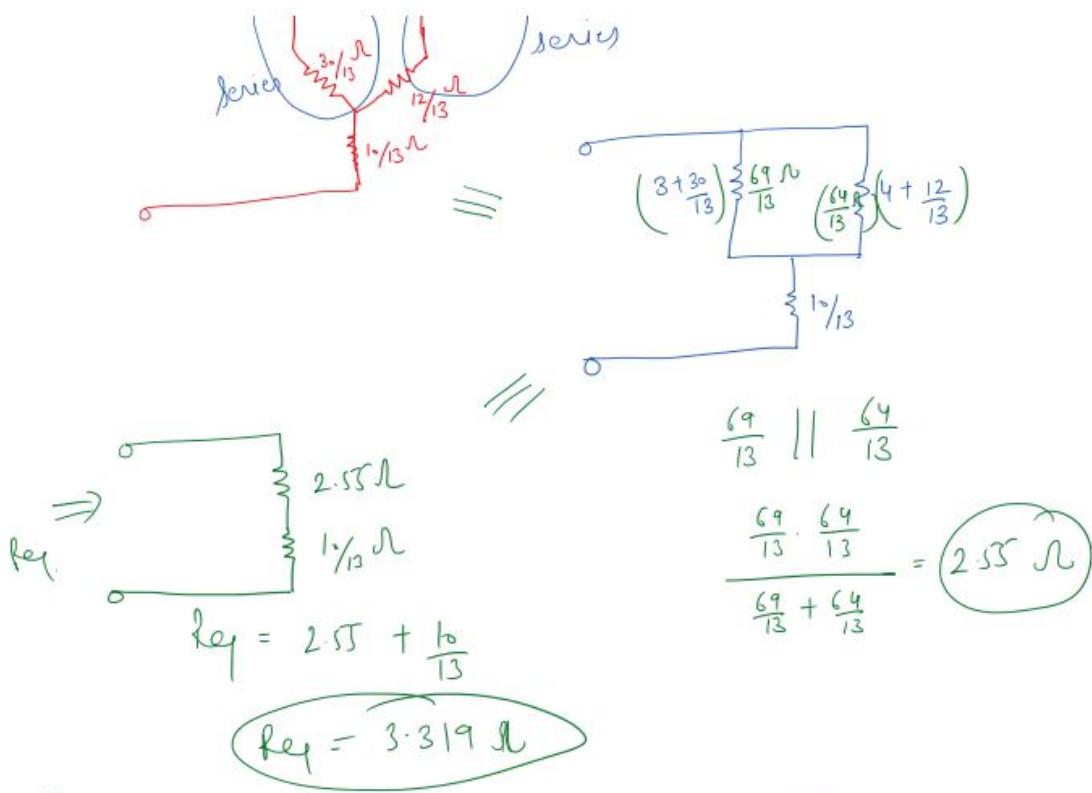

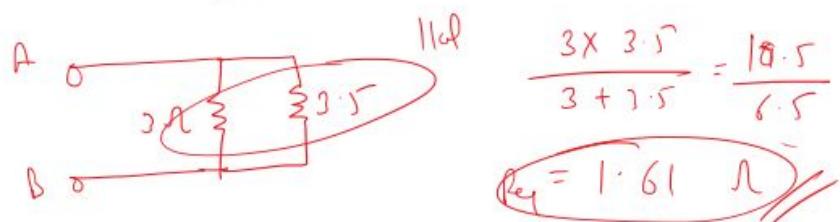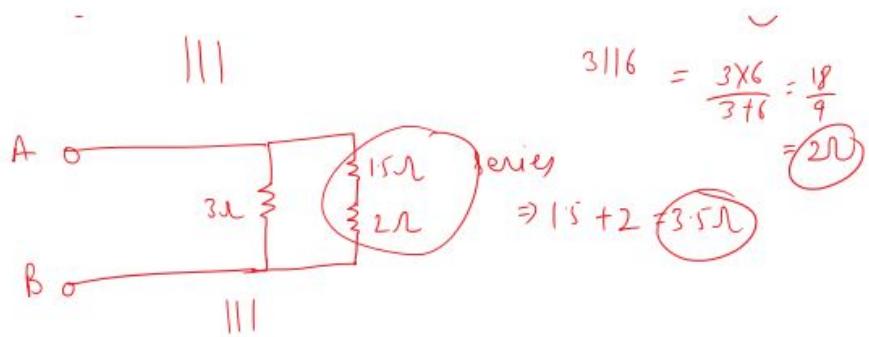

- * When Resistance of Equal Value transformed from star to delta, Resistors increased by 3 times.

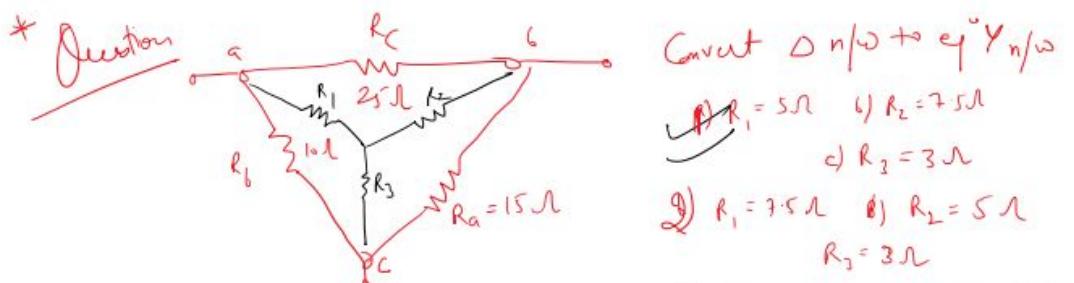- * When Capacitors of equal Value transformed from star to delta, Capacitance decreased by 3 times.



Ques: Delta + Star

$$R_1 = \frac{(25)(1)}{25+10+15} = \frac{250}{50} = 5\Omega$$


$$R_2 = \frac{(25)(15)}{50} = \frac{375}{50} = 7.5\Omega$$

$$R_3 = \frac{(15)(10)}{50} = \frac{150}{50} = 3\Omega$$


* Ans:-



Obtain eq resistance

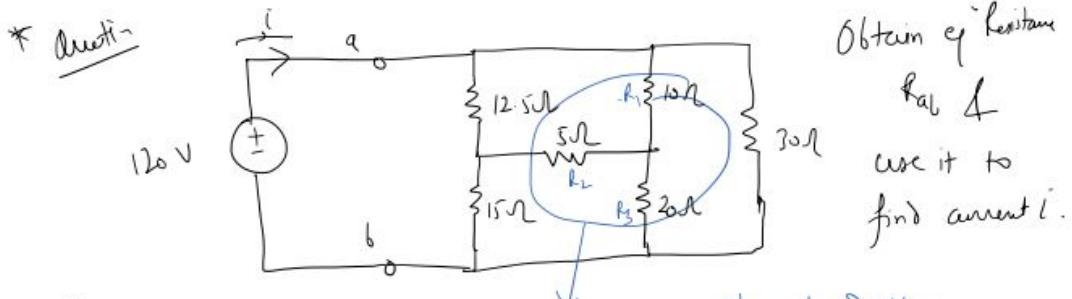

Soln Star to Delta

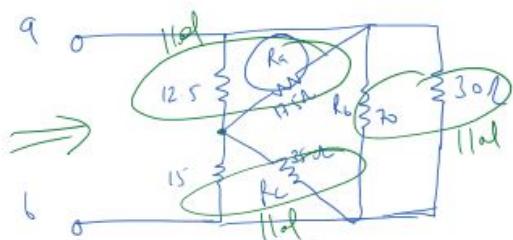

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_a = \frac{50 + 100 + 200}{20}$$



$$R_a = 35 \Omega$$

$$R_b = \frac{35}{5} = 7 \Omega \quad R_c = \frac{35}{10} = 3.5 \Omega$$

$$\rightarrow 12.5 \parallel 11.75 = 7.29 \Omega$$

$$\rightarrow 15 \parallel 35 = 10.5 \Omega$$
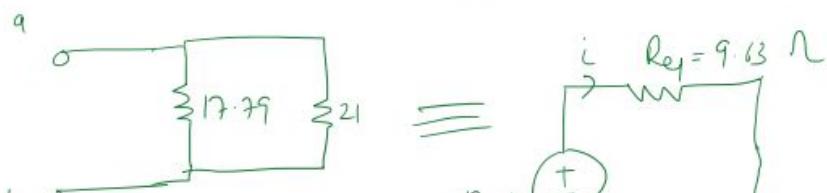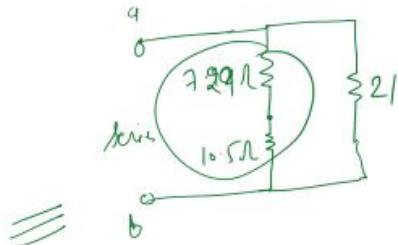
$$\rightarrow 7 \parallel 3.5 = 2.1 \Omega$$



$$\text{Ans} \rightarrow i = \frac{V}{R} = \frac{120}{9.63} = 12.46 \text{ A}$$